


Question 1(a) [3 marks]

Draw and Explain the V-I Characteristics of TRIAC.

Answer:

TRIAC (Triode for Alternating Current) is a bidirectional three-terminal semiconductor device that can conduct current in either direction when triggered.

Diagram:

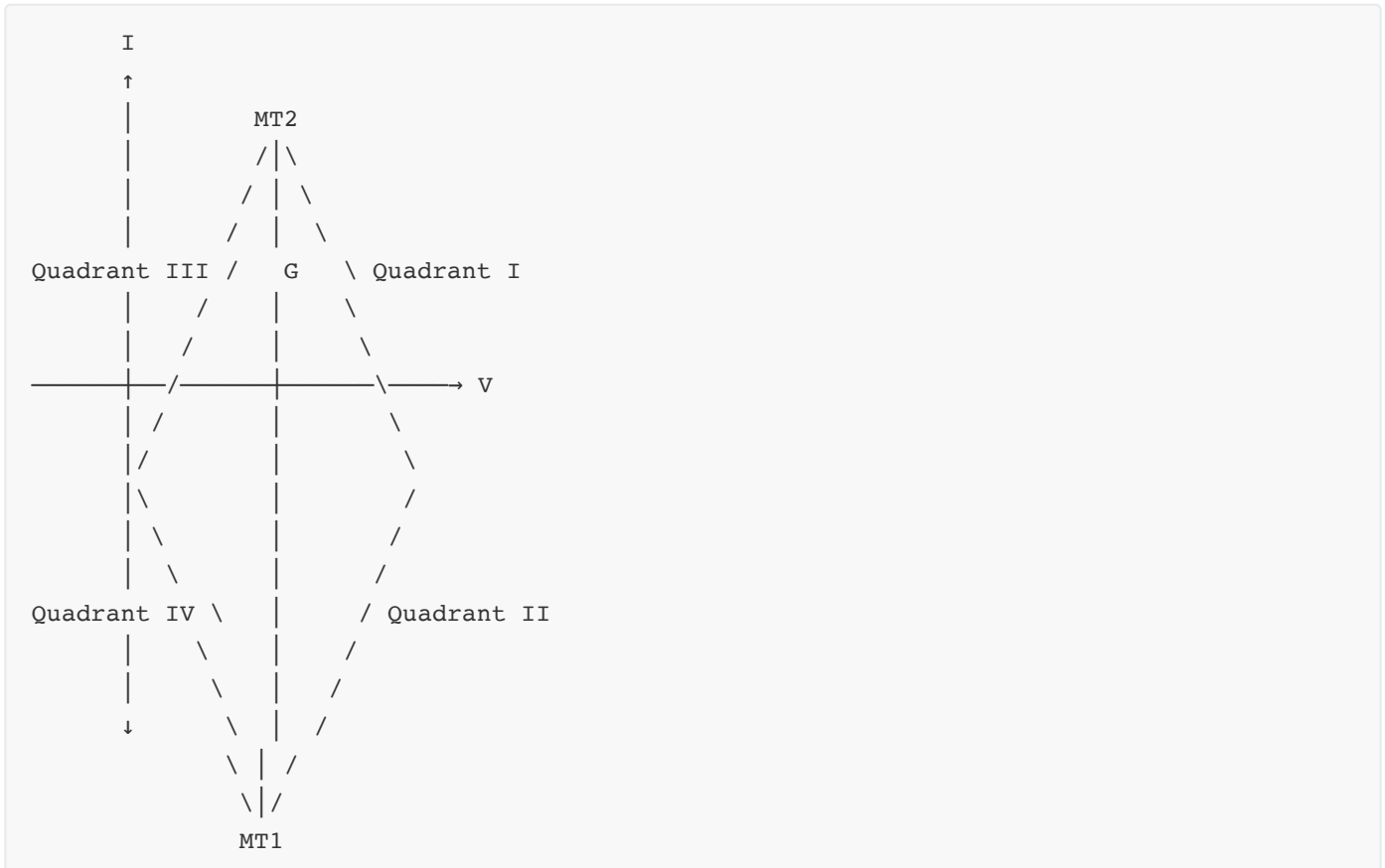

- **Bidirectional operation:** TRIAC conducts in both directions (positive and negative half cycles)
- **Quadrant operation:** Functions in all four quadrants based on polarity of MT2 and gate
- **Triggering voltage:** Breakdown occurs at $\pm V_{BO}$ in either direction
- **Holding current:** Minimum current to maintain conduction

Mnemonic: "Two Rectifiers In A Case"


Question 1(b) [4 marks]

Explain working of SCR using two transistor analogy.

Answer:

SCR (Silicon Controlled Rectifier) can be represented as interconnected PNP and NPN transistors.

Diagram:

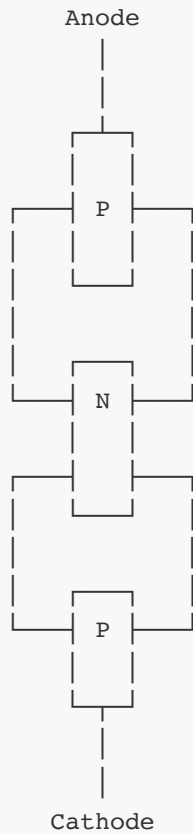

- **Two-transistor structure:** PNP (Q1) and NPN (Q2) connected such that collector of each transistor drives the base of other
- **Regenerative feedback:** Once both transistors start conducting, they keep each other in saturation
- **Triggering:** Applying gate current to Q2 base starts the regenerative process
- **Latching:** Once triggered, SCR remains ON even if gate signal is removed

Mnemonic: "Pull Neat Path"


Question 1(c) [7 marks]


Draw the circuit diagram of photo electric relay using LDR and explain its Working.

Answer:

A photoelectric relay using LDR (Light Dependent Resistor) is a light-activated switching circuit.

Circuit Diagram:

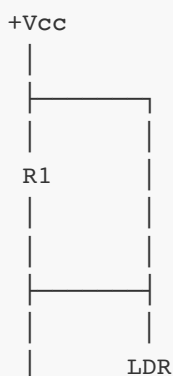

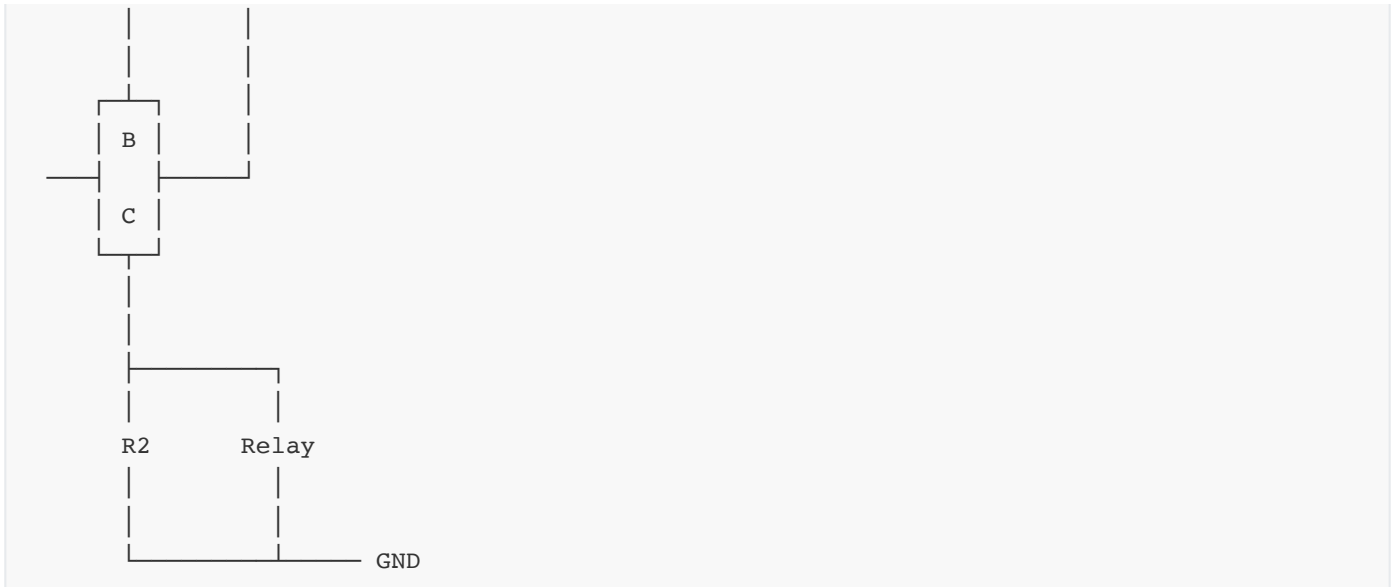

- **Light sensing:** LDR resistance decreases in presence of light
- **Transistor operation:** When light falls on LDR, voltage at transistor base changes
- **Relay switching:** Transistor conducts/cuts off based on light, activating/deactivating relay
- **Threshold adjustment:** Potentiometer R1 sets light sensitivity level
- **Applications:** Automatic street lights, burglar alarms, automatic door openers

Mnemonic: "Light Detects Readily"


Question 1(c OR) [7 marks]


Draw the gate pulse trigger circuit using UJT for SCR and explain its working.

Answer:

UJT (Unijunction Transistor) provides reliable trigger pulses for SCR.

Circuit Diagram:

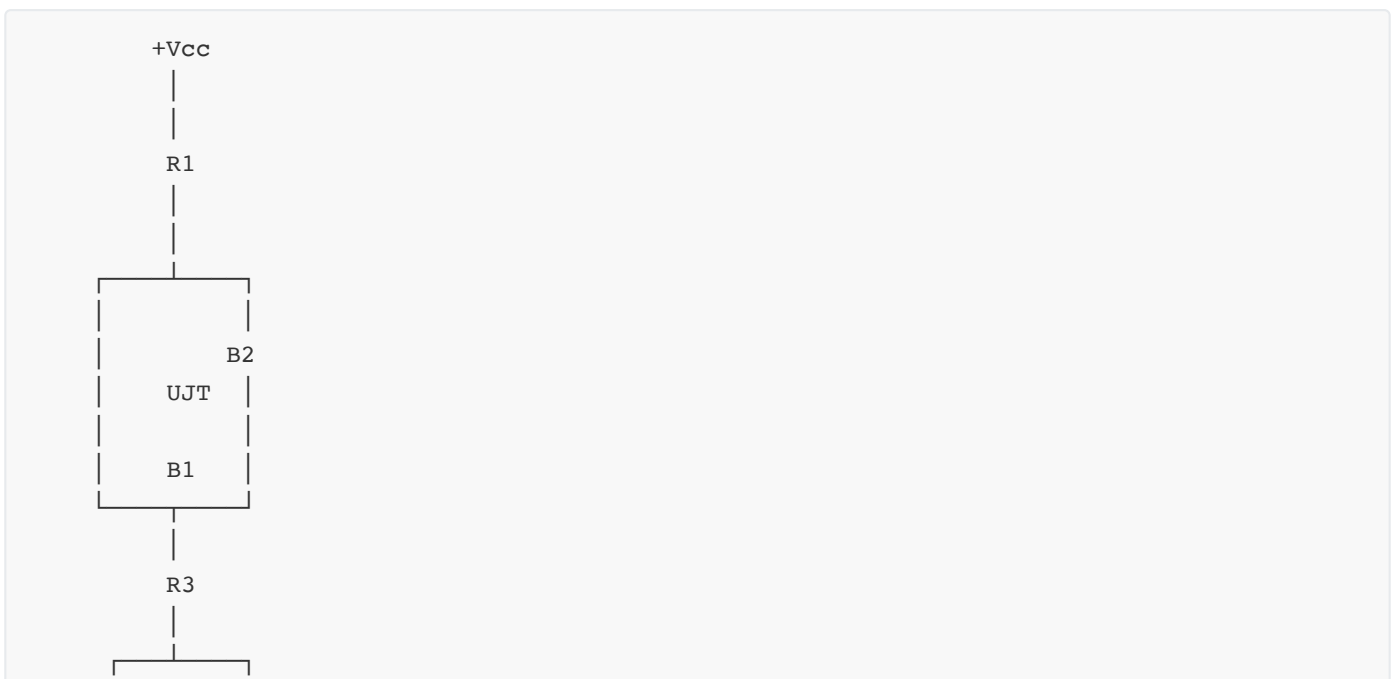

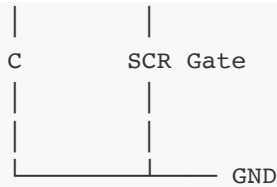

- **RC timing:** R1 and C form charging circuit that determines pulse frequency
- **UJT operation:** UJT fires when capacitor voltage reaches peak point voltage
- **Pulse generation:** UJT discharges capacitor producing sharp trigger pulse
- **SCR triggering:** Pulse applied to SCR gate turns it ON at specific points in AC cycle
- **Frequency control:** Adjusting R1 changes pulse frequency for phase control

Mnemonic: "Uniform Junctions Trigger"

Question 2(a) [3 marks]

State Triggering methods of SCR.

Answer:

| Triggering Method | Operating Principle | Advantages |
|----------------------------|------------------------------------|--------------------------------------|
| Gate Triggering | Current applied to gate terminal | Most common, precise control |
| Thermal Triggering | Temperature rise causes leakage | Simple, no external circuit |
| Light Triggering | Photons create electron-hole pairs | Electrical isolation, used in LASCRs |
| dv/dt Triggering | Rapid voltage rise causes turn-on | Useful for protection circuits |
| Forward Voltage Triggering | Exceeding breakover voltage | No gate connection needed |

Mnemonic: "Good Triggers Let Devices Fire"


Question 2(b) [4 marks]

What is Commutation of SCR? Explain class-E commutation.

Answer:

Commutation is the process of turning OFF an SCR by reducing its anode current below holding current.

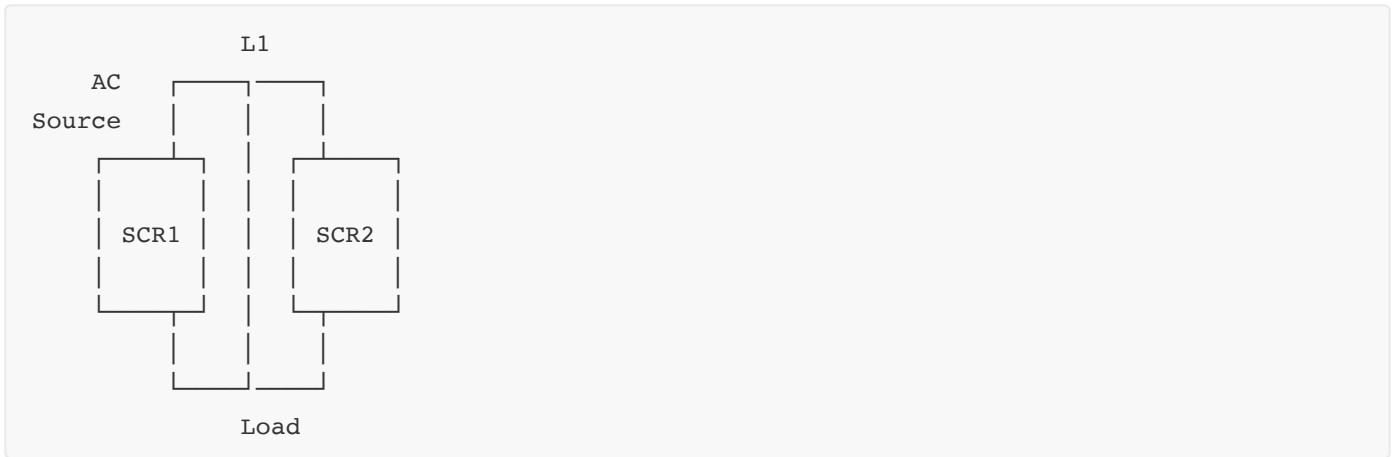Class-E Commutation (Complementary Commutation):



- **Complementary switching:** Uses another SCR in opposite half-cycle
- **Natural commutation:** AC source crosses zero, anode current falls below holding current
- **Application:** AC power control circuits, cycloconverters
- **Advantage:** No additional commutation components required

Mnemonic: "Complementary Elements"


Question 2(c) [7 marks]

Draw and explain Snubber Circuit for SCR.

Answer:

A snubber circuit protects SCR from voltage transients and dv/dt turn-on.

Circuit Diagram:

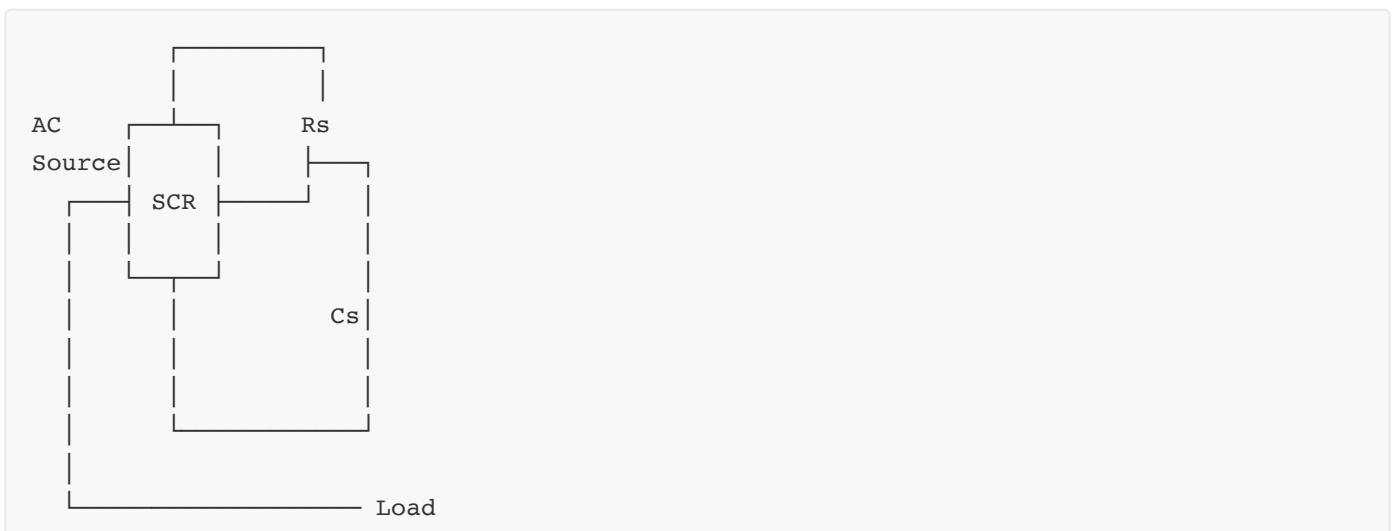

- **RC network:** Series resistor (R_s) and capacitor (C_s) connected across SCR
- **Transient suppression:** Capacitor absorbs voltage spikes that could damage SCR
- **dv/dt protection:** Prevents false triggering due to rapid voltage rise
- **Turn-off assistance:** Helps in commutation by providing alternate current path
- **Component selection:** C_s based on load current, R_s limits discharge current

Mnemonic: "Safely Neutralizes Unwanted Breakover"

Question 2(a OR) [3 marks]

Explain over current protection method of SCR.

Answer:

| Protection Method | Working Principle | Applications |
|-----------------------------|-----------------------------------|-------------------------------|
| Fuses | Melts when current exceeds rating | Simple, economical protection |
| Circuit Breakers | Trips on overload, can be reset | Reusable protection |
| Current Limiting Reactors | Limits fault current magnitude | Industrial power control |
| Electronic Current Limiting | Senses current and controls gate | Precise protection |
| Crowbar Circuit | Shorts power supply on overload | Protects sensitive loads |

Mnemonic: "Fault Current Causes Equipment Damage"


Question 2(b OR) [4 marks]

Explain the working of opto-SCR.

Answer:

An opto-SCR (or Light Activated SCR) combines a light source and SCR in an isolated package.

Diagram:

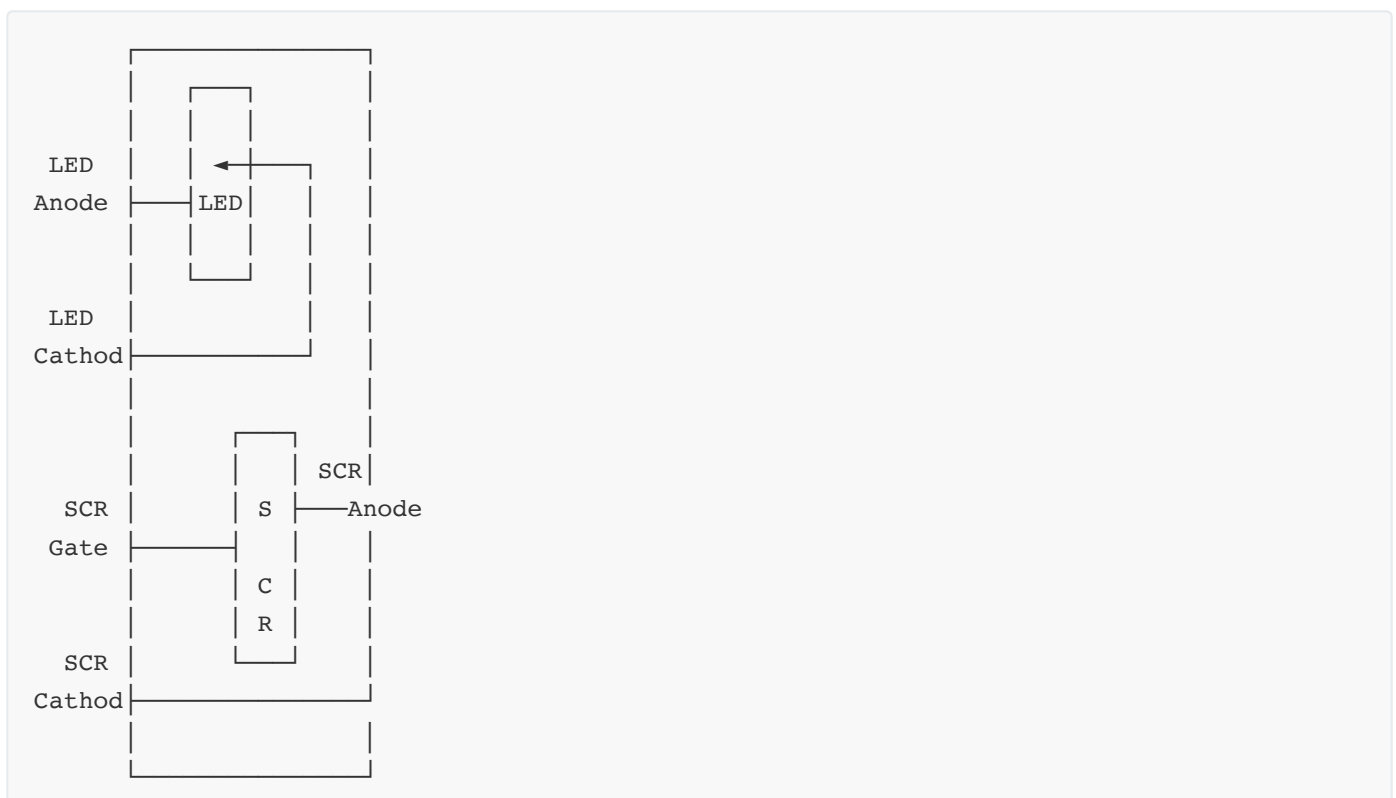

- **Electrical isolation:** LED optically triggers SCR without electrical connection
- **Noise immunity:** Immune to electrical noise and interference
- **High-voltage isolation:** Separates control and power circuits
- **Applications:** Industrial control, high-voltage switching

Mnemonic: "Light Activates Silicon Control"


Question 2(c OR) [7 marks]

What is force commutation? Explain any two.

Answer:


Force commutation is artificially turning OFF an SCR by reducing its anode current below holding level.

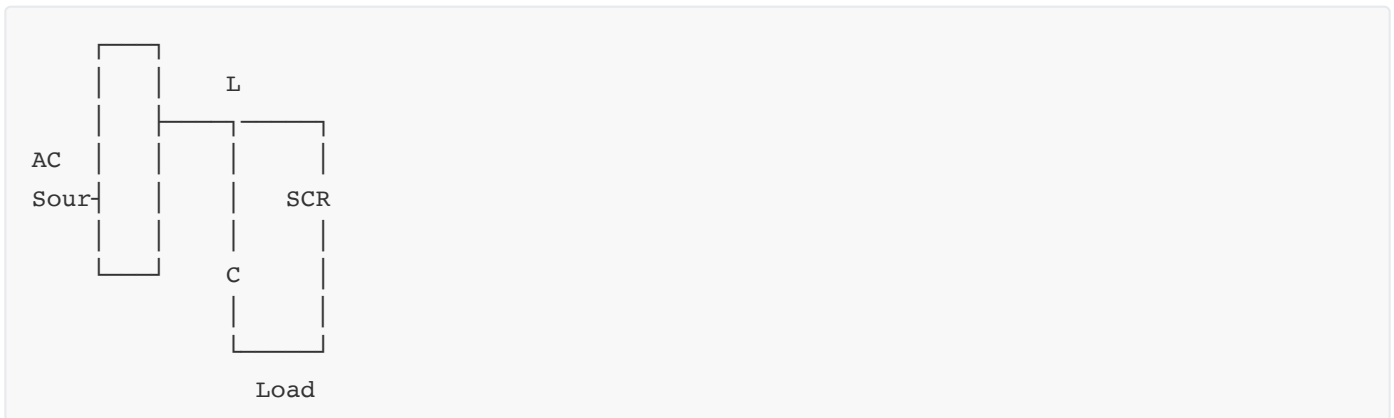1. Class A Commutation (Self-Commutation):



- **LC resonant circuit:** Parallel L-C across SCR creates oscillations
- **Reverse current:** L-C circuit forces reverse current through SCR
- **Applications:** Inverters, choppers

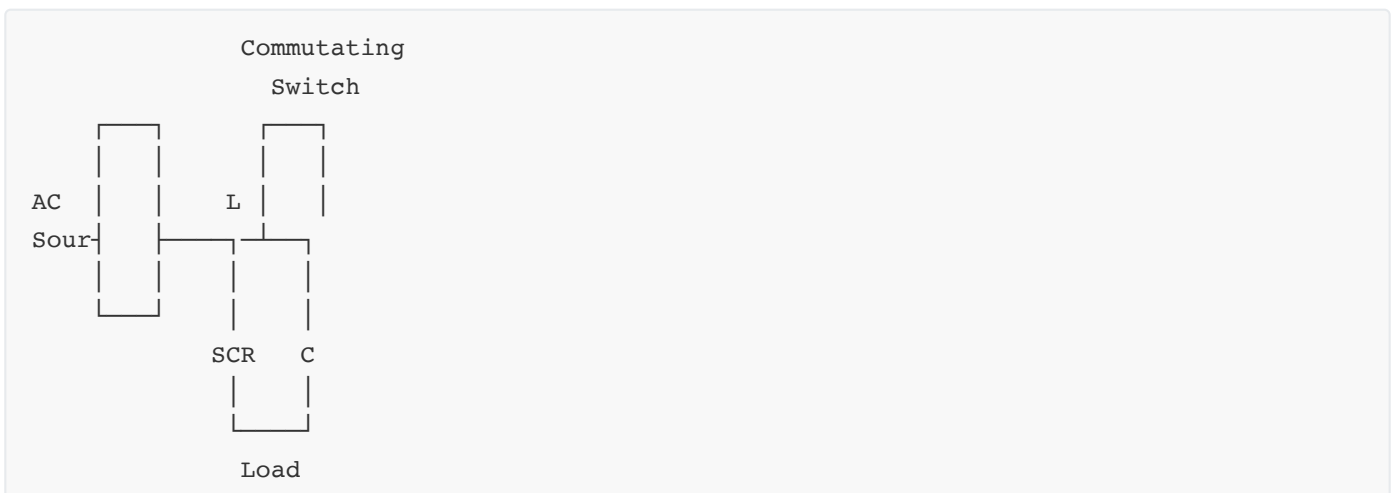2. Class B Commutation (Resonant Pulse Commutation):



- **External switch:** Additional SCR or switch triggers commutation
- **Energy storage:** L-C circuit stores energy then reverses SCR current

- **Applications:** DC choppers, controlled rectifiers

Mnemonic: "Force Circuit Reversal"


Question 3(a) [3 marks]

Explain 1- ϕ full Wave bridge-controlled rectifier using four diodes & one SCR.

Answer:

This circuit combines diodes and an SCR for controlled single-phase full-wave rectification.

Circuit Diagram:

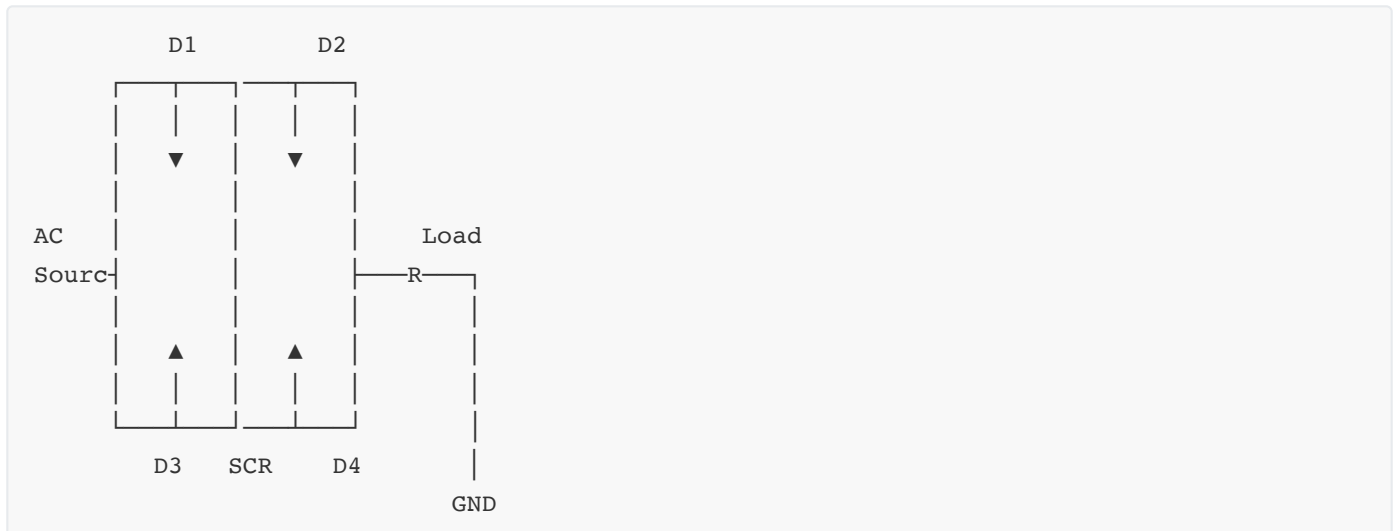

- **Bridge configuration:** Four diodes arranged in bridge with one replaced by SCR
- **Variable output:** SCR controls conduction angle and thus output voltage
- **Economical design:** Uses only one SCR instead of two or four
- **Efficiency:** Higher than half-wave controlled rectifier

Mnemonic: "Blend Diodes Smartly"

Question 3(b) [4 marks]

What is Chopper? What are its application?

Answer:

| Aspect | Description |
|-------------------|---|
| Definition | DC-DC converter that converts fixed DC input to variable DC output |
| Working Principle | Periodically switches DC input ON/OFF at high frequency |
| Types | Step-down (Buck), Step-up (Boost), Buck-Boost, Cuk |
| Control Methods | PWM, Frequency modulation, Current-limit control |
| Applications | DC motor speed control, Battery chargers, UPS, Solar systems, Electric vehicles |

Mnemonic: "Chops Current Perfectly"


Question 3(c) [7 marks]

Draw and explain the circuit diagram of static switch using SCR for 1- ϕ A.C. Load.

Answer:

A static switch using SCR provides non-mechanical switching for AC loads.

Circuit Diagram:

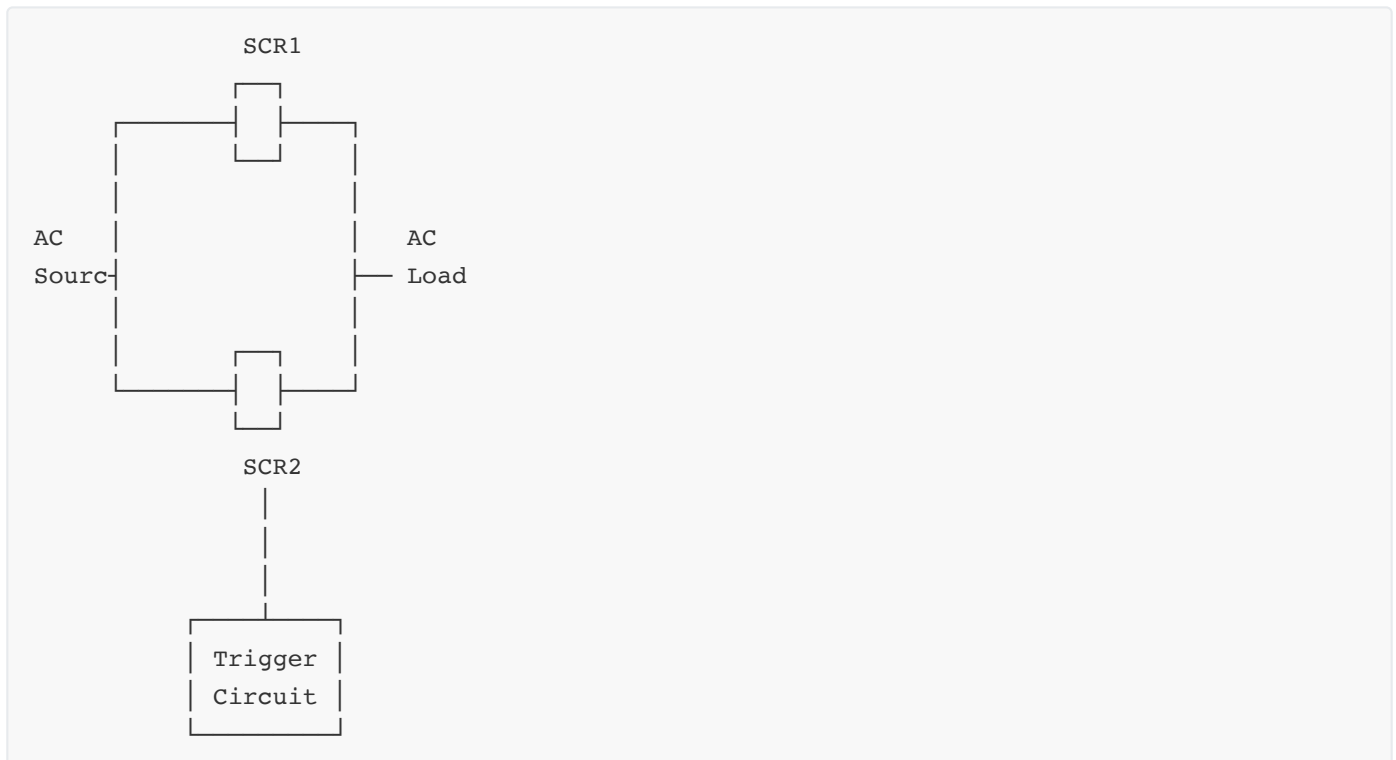

- **Antiparallel SCRs:** Two SCRs connected in inverse parallel for bidirectional conduction
- **Gate control:** Properly timed gate signals control power to load
- **Zero-crossing switching:** SCRs naturally turn OFF at zero crossing
- **Applications:** Heater control, motor soft-starting, lighting control
- **Advantages:** No moving parts, silent operation, long life

Mnemonic: "Solid Switching Technology"

Question 3(a OR) [3 marks]

Explain basic principle of DC Chopper.

Answer:

| Component | Function |
|-------------------|---|
| Switching Device | SCR, MOSFET, IGBT switches DC at high frequency |
| Control Circuit | Generates PWM gate signals to control ON/OFF time |
| Duty Cycle | Ratio of ON time to total time period determines output |
| Output Filter | Smooths chopped output to reduce ripple |
| Working Principle | Average voltage = Input voltage × Duty cycle |

Mnemonic: "Direct Current Control"


Question 3(b OR) [4 marks]

Write short note on: Un-interrupted Power Supply (UPS).

Answer:

UPS provides emergency power when main supply fails.

Block Diagram:

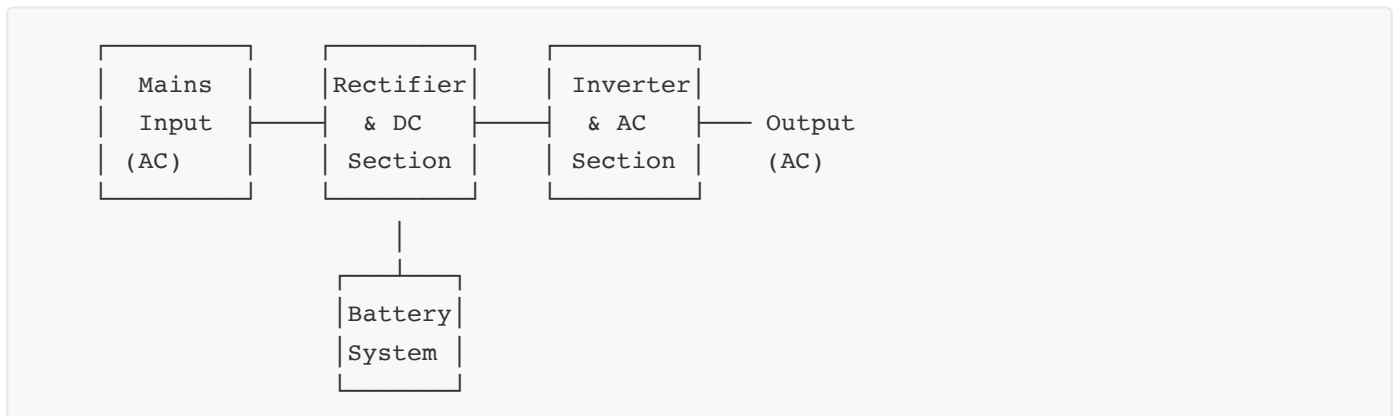

- **Backup power:** Provides continuous power during outages
- **Types:** Online, Offline, Line-interactive UPS
- **Protection:** Against power surges, sags, and frequency variations
- **Applications:** Computers, medical equipment, telecommunications

Mnemonic: "Uninterrupted Power Securely"


Question 3(c OR) [7 marks]

Draw the block diagram of SMPS and explain the function of each block.

Answer:

Switched-Mode Power Supply converts AC to regulated DC efficiently.

Block Diagram:

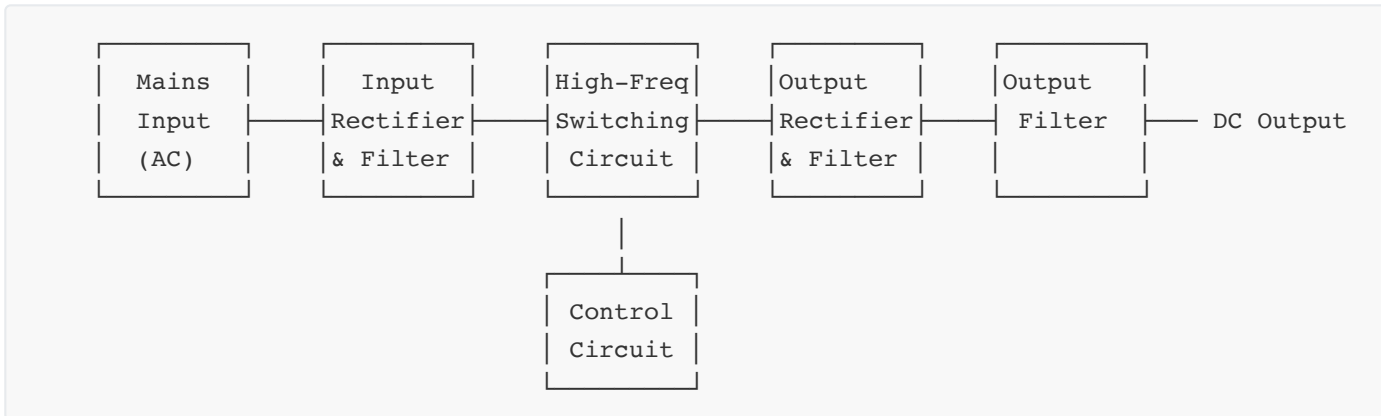

- **Input rectifier:** Converts AC to unregulated DC
- **High-frequency switching:** Converts DC to high-frequency AC using transistors
- **Transformer:** Provides isolation and voltage scaling
- **Output rectifier:** Converts high-frequency AC to DC
- **Filter:** Smooths DC output to reduce ripple
- **Control circuit:** Regulates output through feedback

Mnemonic: "Switch Mode Power System"


Question 4(a) [3 marks]

Draw the circuit diagram using TRIAC for speed control of 1- ϕ DC Shunt motor and Explain its working.

Answer:

TRIAC-based speed control for a DC shunt motor provides efficient variable speed.

Circuit Diagram:

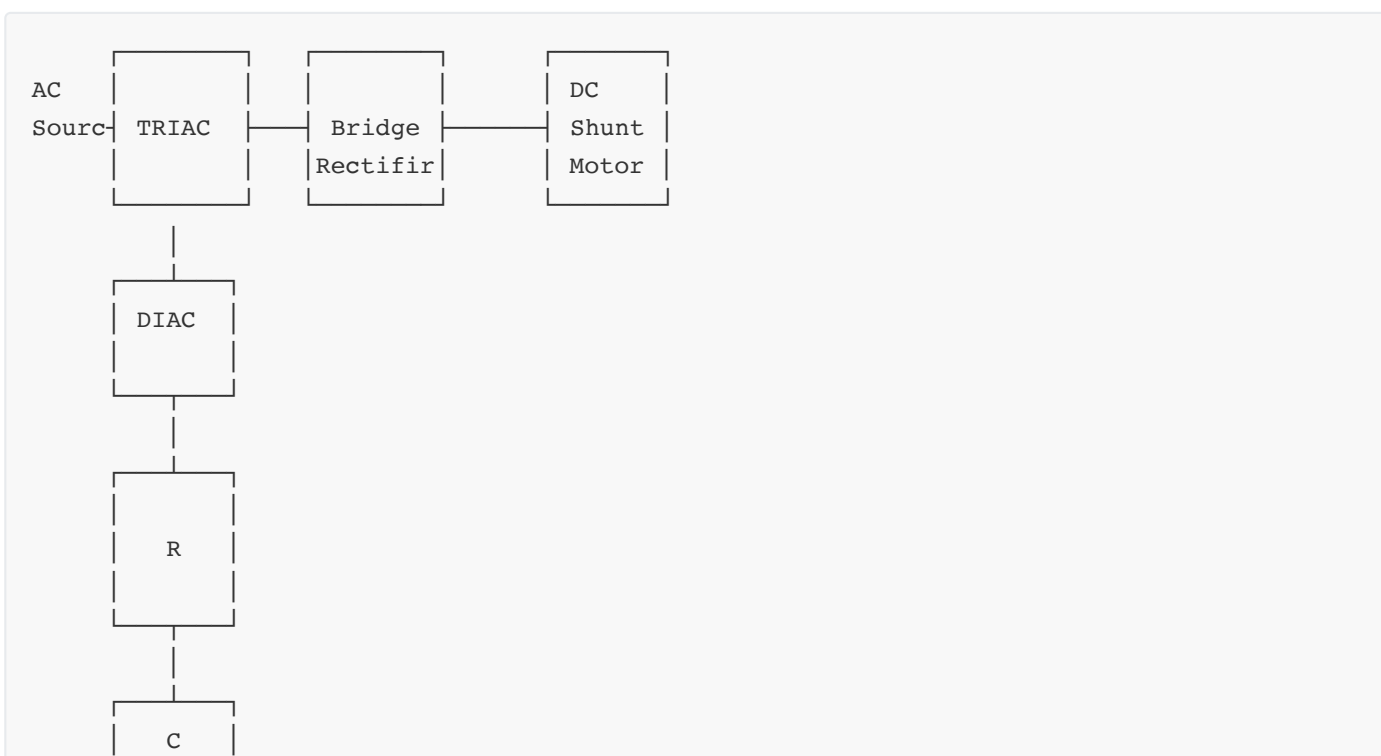



- **Phase control:** TRIAC varies effective voltage through phase angle control
- **Rectification:** Bridge rectifier converts AC to DC for motor
- **Speed variation:** Motor speed proportional to applied voltage
- **RC timing:** RC network determines firing angle of TRIAC

Mnemonic: "TRIAC Regulates Speed"


Question 4(b) [4 marks]

Draw and explain the circuit diagram four stage sequential timer using IC-556.

Answer:

IC-556 dual timer can be configured as a multi-stage sequential timer.

Circuit Diagram:

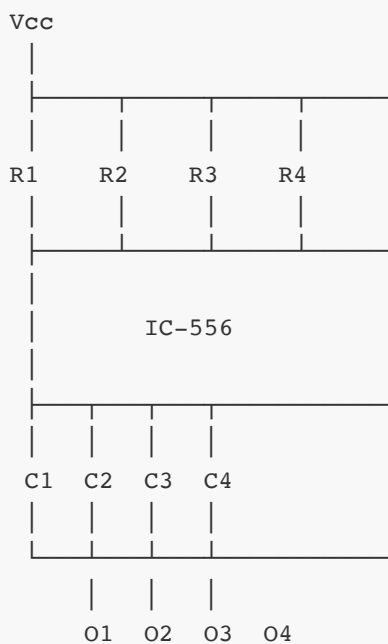

- **Dual timer IC:** IC-556 contains two 555 timer circuits
- **Cascaded configuration:** Output of one stage triggers the next
- **Timing control:** RC time constants determine duration of each stage
- **Applications:** Industrial sequencing, process control, automation

Mnemonic: "Sequential Steps Timed Precisely"


Question 4(c) [7 marks]

Explain induction heating.

Answer:

Induction heating is a non-contact heating process using electromagnetic induction.

Diagram:

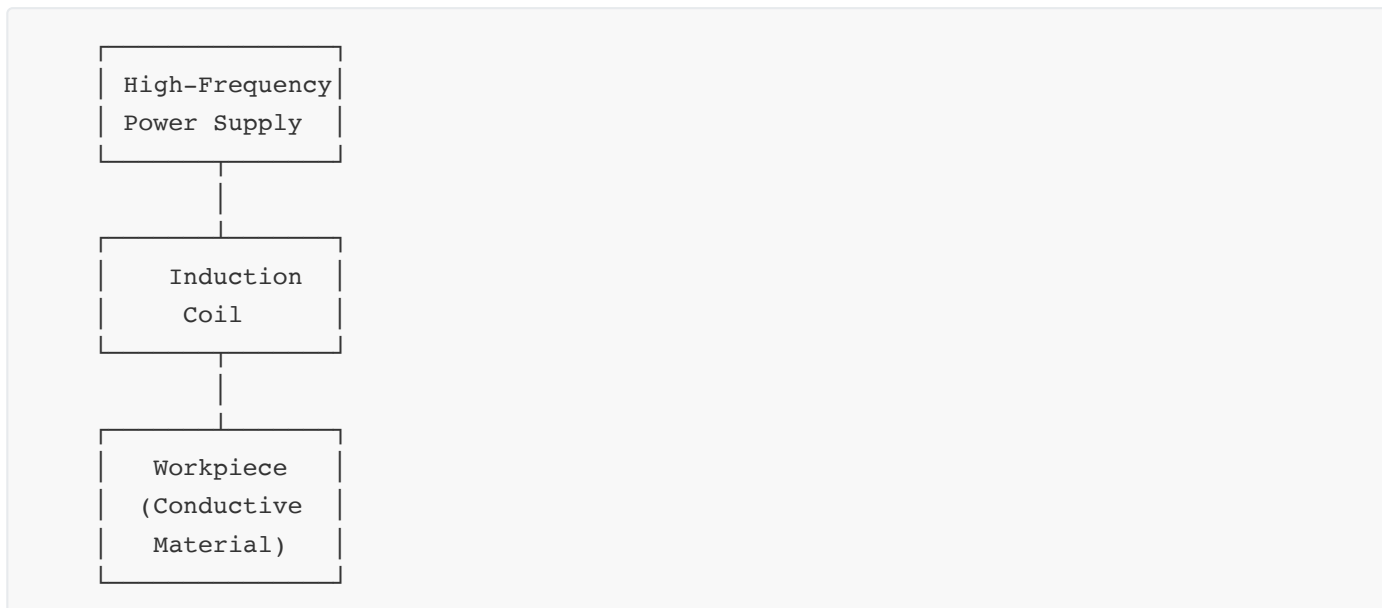

| Principle | Description |
|---------------------------|--|
| Electromagnetic Induction | AC in coil creates alternating magnetic field |
| Eddy Currents | Magnetic field induces currents in workpiece |
| Resistive Heating | Eddy currents generate heat due to material resistance |
| Skin Effect | Current concentrates near surface at high frequencies |
| Applications | Heat treatment, melting, forging, brazing, cooking |

Mnemonic: "Induced Heating Efficiently"


Question 4(a OR) [3 marks]


Draw and explain three stage IC555 timer circuit.

Answer:

A three-stage timer using IC555 provides sequential timing operations.

Circuit Diagram:

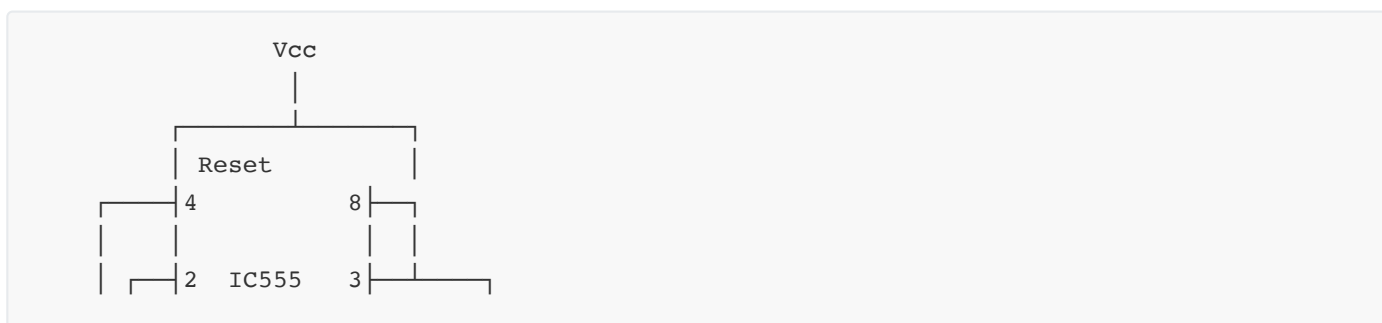

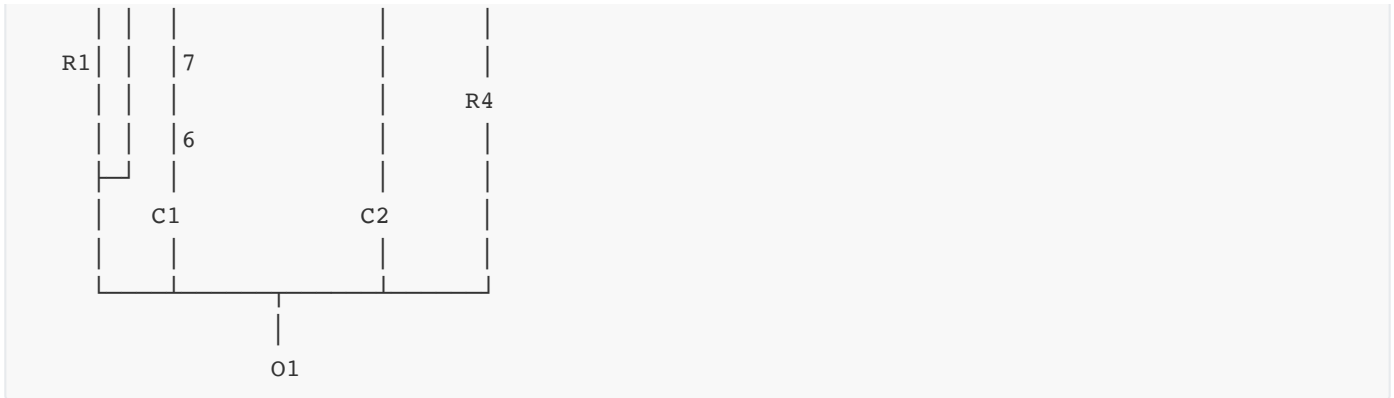

- **Monostable mode:** Each stage operates in monostable mode with fixed time delay
- **Cascaded connection:** Output of first timer triggers second, and so on
- **Timing components:** R-C network determines time delay of each stage
- **Applications:** Automatic sequencing, process timing, industrial control

Mnemonic: "Time Intervals Created"

Question 4(b OR) [4 marks]

Explain the principle of dielectric heating.

Answer:

| Principle | Description |
|-------------------------------|--|
| High-Frequency Electric Field | Material placed between electrodes with RF voltage (1-100 MHz) |
| Molecular Friction | Dipole molecules vibrate/rotate trying to align with alternating field |
| Heat Generation | Internal friction between molecules generates heat uniformly |
| Non-Conductive Materials | Effective for heating non-conductive materials (plastics, wood, food) |
| Applications | Plastic welding, wood drying, food processing (microwave ovens) |

Mnemonic: "Dielectric Energy Heats"

Question 4(c OR) [7 marks]

Make comparison between Induction heating and Dielectric heating.

Answer:

| Parameter | Induction Heating | Dielectric Heating |
|--------------------|--|---|
| Basic Principle | Electromagnetic induction | High-frequency electric field |
| Suitable Materials | Conductive materials (metals) | Non-conductive materials (plastics, wood) |
| Frequency Range | 1 kHz to 1 MHz | 1 MHz to 1 GHz |
| Heating Mechanism | Eddy currents and hysteresis | Molecular friction (dipole rotation) |
| Heat Distribution | Surface heating (skin effect) | Volumetric (uniform throughout) |
| Efficiency | 80-90% for magnetic materials | 50-70% depending on material |
| Applications | Metal melting, forging, heat treatment | Plastic welding, food processing, drying |
| Equipment | Induction coil, work piece | Electrodes, dielectric material |

Mnemonic: "ICED" - Induction Conductive, Eddy currents; Dielectric, Dipoles


Question 5(a) [3 marks]

Explain Construction and working of Universal Motor.

Answer:

Universal motor operates on both AC and DC power sources.

Diagram:

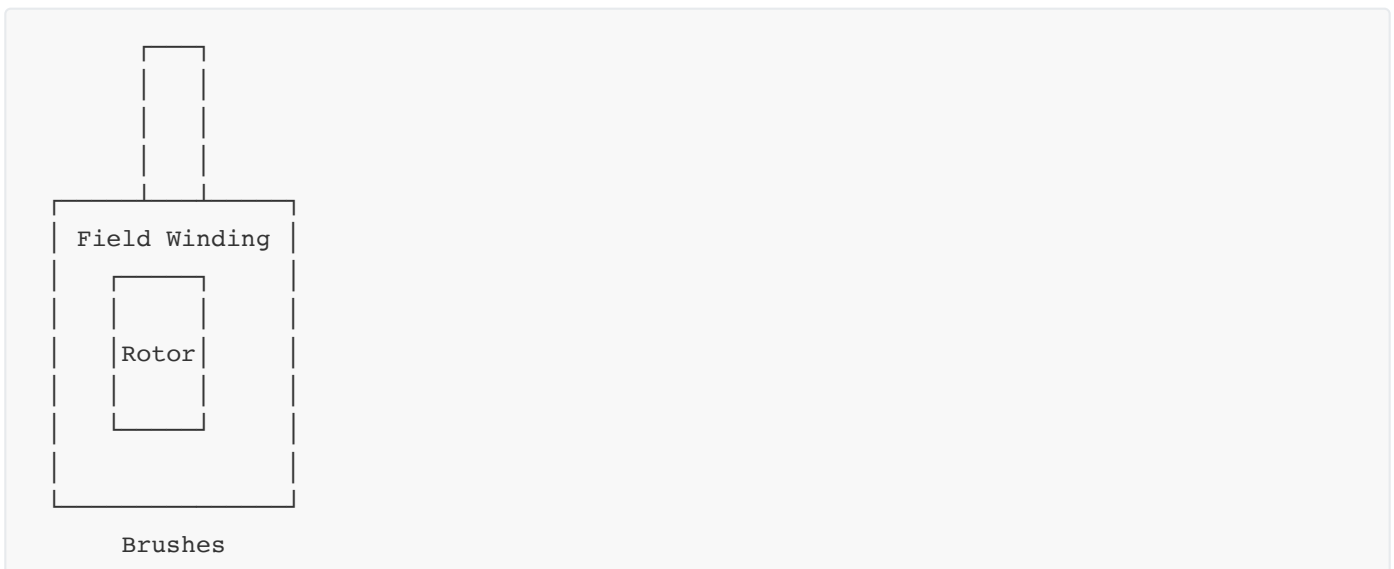

- **Series connection:** Field winding in series with armature winding
- **Construction:** Stator with field winding, rotor with commutator and brushes
- **Operating principle:** Same direction torque on both AC and DC

- **Characteristics:** High starting torque, high speed at low load
- **Applications:** Portable tools, household appliances, blenders

Mnemonic: "Universally Motorized"


Question 5(b) [4 marks]

Draw and explain the construction of DC servo motor.

Answer:

DC servo motor provides precise position or speed control.

Diagram:

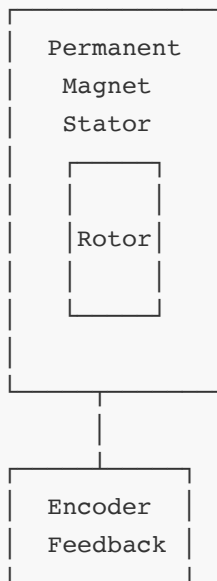

- **Construction:** Permanent magnet stator, lightweight rotor, feedback device
- **Control system:** Closed-loop control with position/velocity feedback
- **Low inertia:** Allows quick response and precise positioning
- **Applications:** Robotics, CNC machines, positioning systems
- **Features:** High torque-to-inertia ratio, fast response, accuracy

Mnemonic: "Servo System Control"


Question 5(c) [7 marks]

Draw the block diagram of Programmable logic Control (PLC) and explain the Function of each block.

Answer:

PLC is an industrial digital computer for automation control.

Block Diagram:

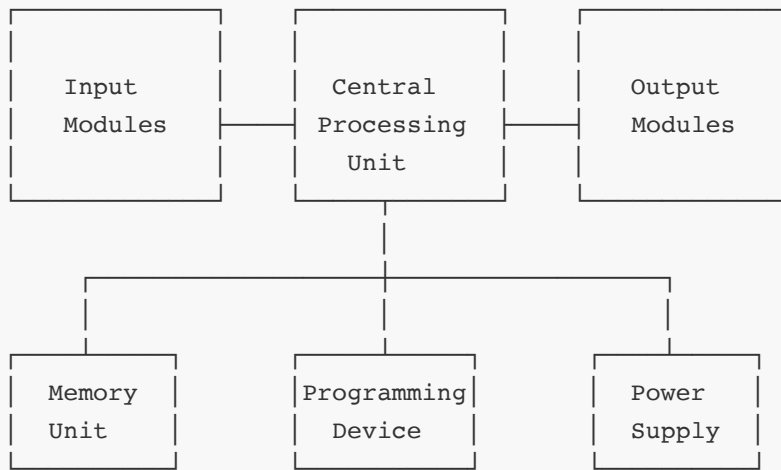

- **CPU (Central Processing Unit):** Executes program, processes I/O data, makes decisions
- **Input modules:** Convert field signals (sensors, switches) to digital signals for CPU
- **Output modules:** Convert CPU commands to actuator signals (motors, valves)
- **Memory unit:** Stores program and data (ROM for OS, RAM for user program)
- **Programming device:** PC or console for program development and monitoring
- **Power supply:** Provides regulated power to PLC components

Mnemonic: "Programs Logic Completely"


Question 5(a OR) [3 marks]

Draw and explain the construction of Stepper motor.

Answer:

Stepper motor rotates in discrete steps for precise positioning.

Diagram:

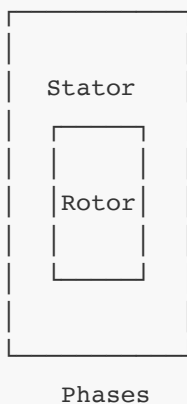

- **Stator:** Contains multiple coil windings (phases)
- **Rotor:** Permanent magnet or variable reluctance type
- **Types:** Permanent magnet, variable reluctance, hybrid

- **Step angle:** Typically 1.8° (200 steps/rev) or 0.9° (400 steps/rev)
- **Applications:** Printers, disk drives, robotics, CNC machines

Mnemonic: "Steps Precisely Moved"


Question 5(b OR) [4 marks]

Draw explain solid state circuit to control DC shunt Motor Speed.

Answer:

Solid-state circuit provides efficient and smooth DC motor speed control.

Circuit Diagram:

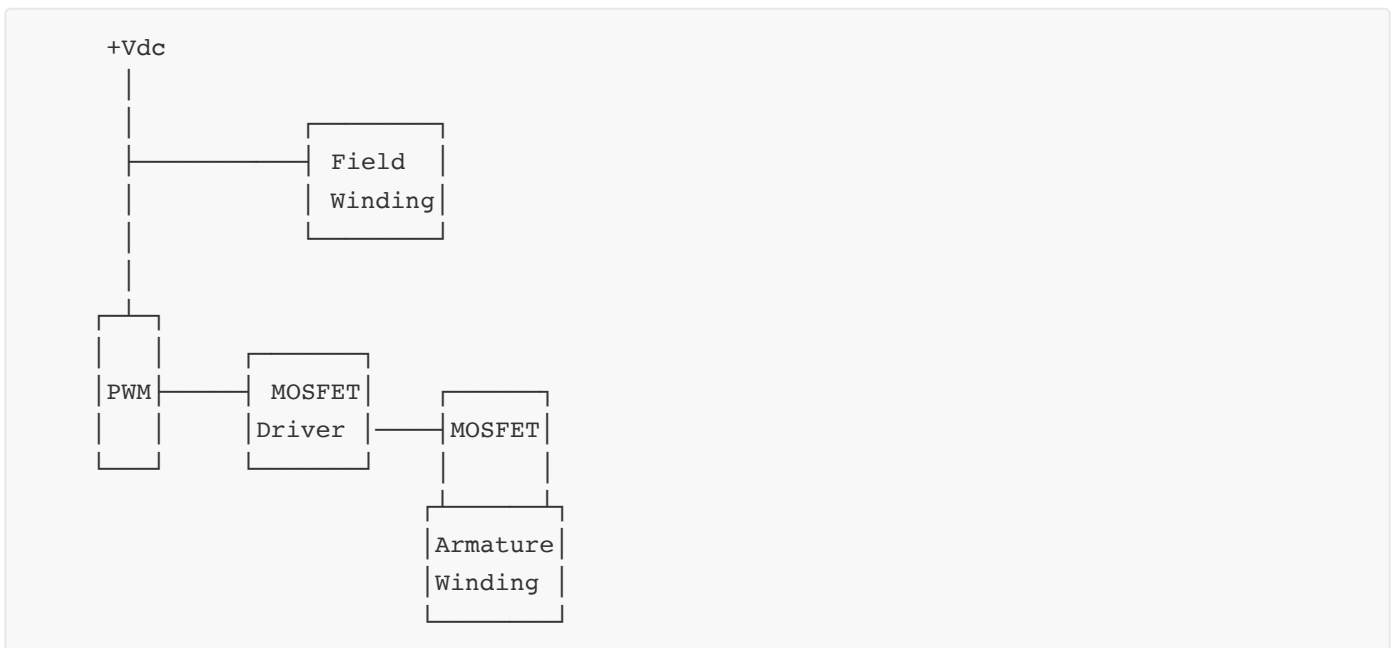

- **PWM controller:** Generates variable duty cycle pulses to control speed
- **MOSFET driver:** Provides gate drive to power MOSFET
- **Power MOSFET:** Controls current through armature winding
- **Feedback:** Tachogenerator or encoder provides speed feedback
- **Advantages:** Efficient, smooth control, wide speed range

Mnemonic: "Power With MOSFET"


Question 5(c OR) [7 marks]

Explain the Working of VFD (Variable Frequency Drive).

Answer:

VFD controls AC motor speed by varying frequency and voltage.

Block Diagram:

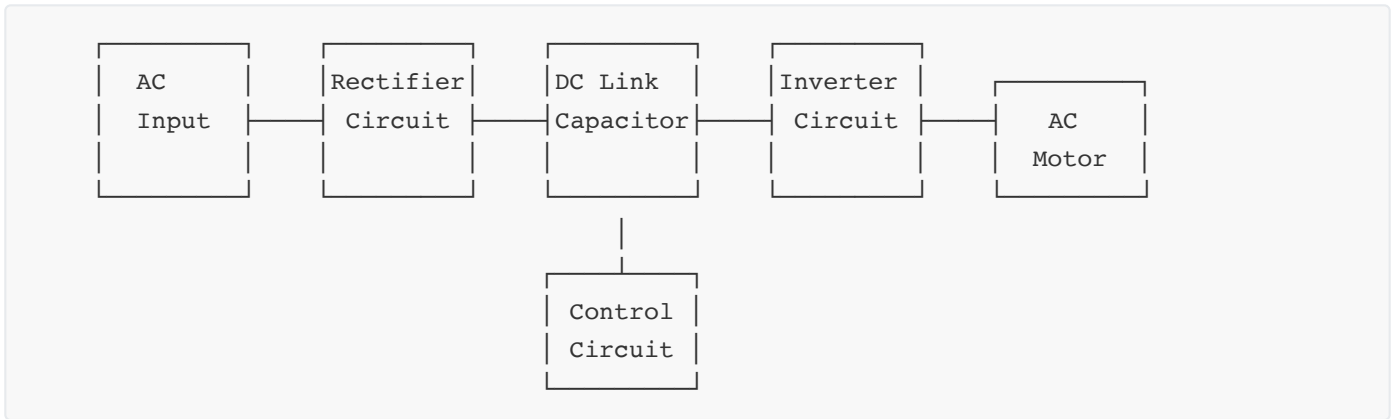

| Component | Function |
|-----------------|--|
| Rectifier | Converts AC input to DC (diode bridge or active front end) |
| DC Link | Filters DC and stores energy (capacitors, sometimes inductors) |
| Inverter | Converts DC to variable frequency AC (IGBTs with PWM) |
| Control Circuit | Regulates frequency/voltage based on speed requirement |
| Braking Circuit | Dissipates regenerative energy during deceleration |

- **Speed control:** Motor speed proportional to frequency ($\text{RPM} = 120f/P$)
- **Torque control:** Maintains V/f ratio for constant torque
- **Energy savings:** Reduces energy consumption at lower speeds
- **Applications:** Pumps, fans, conveyors, process control
- **Features:** Soft start, overcurrent protection, regenerative braking

Mnemonic: "Vary Frequency, Drive motor"