 


## Question 1(a) [3 marks]

Draw neat labeled diagram of physical structure of n-channel MOSFET.

Answer:

Diagram:



**Key Components:**

- **Source:** n+ doped region providing electrons
- **Drain:** n+ doped region collecting electrons
- **Gate:** Metal electrode controlling channel
- **Oxide:** SiO<sub>2</sub> insulating layer
- **Substrate:** p-type silicon body


**Mnemonic:** "SOGD - Source, Oxide, Gate, Drain"

## Question 1(b) [4 marks]

Draw energy band diagram of depletion and inversion of MOS under external bias with MOS biasing diagram. Explain inversion region in detail.

Answer:

**MOS Biasing Circuit:**

 

**Energy Band Diagrams:**

Bias Condition	Energy Band Behavior
Depletion	Bands bend upward, holes depleted
Inversion	Strong band bending, electron channel forms

**Inversion Region Details:**

- **Strong inversion:**  $V_G > V_T$  (threshold voltage)
- **Electron channel:** Forms at Si-SiO<sub>2</sub> interface
- **Channel conductivity:** Increases with gate voltage
- **Threshold condition:** Surface potential =  $2\phi_F$

**Mnemonic:** "DIVE - Depletion, Inversion, Voltage, Electrons"

## Question 1(c) [7 marks]


Explain I-V characteristics of MOSFET.

Answer:

**I-V Characteristic Regions:**

Region	Condition	Drain Current
Cutoff	$V_{GS} < V_T$	$I_D \approx 0$
Linear	$V_{GS} > V_T, V_{DS} < V_{GS} - V_T$	$I_D = \mu_n C_{ox} (W/L) [(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$
Saturation	$V_{GS} > V_T, V_{DS} \geq V_{GS} - V_T$	$I_D = (\mu_n C_{ox}/2)(W/L)(V_{GS} - V_T)^2$

**Characteristic Curve:**

 **Key Parameters:**

- $\mu_n$ : Electron mobility
- $C_{ox}$ : Gate oxide capacitance
- $W/L$ : Width to length ratio
- $V_T$ : Threshold voltage

**Operating Modes:**

- **Enhancement:** Channel forms with positive VGS
- **Square law:** Saturation region follows quadratic relationship

**Mnemonic:** "CLS - Cutoff, Linear, Saturation"

**Question 1(c) OR [7 marks]**

**Define scaling. Explain the need of scaling. List and explain the negative effects of scaling.**

**Answer:**

**Definition:**

**Scaling** is the systematic reduction of MOSFET dimensions to improve performance and density.

**Need for Scaling:**

Benefit	Description
Higher Density	More transistors per chip area
Faster Speed	Reduced gate delays
Lower Power	Decreased switching energy
Cost Reduction	More chips per wafer

**Scaling Types:**

Type	Gate Length	Supply Voltage	Oxide Thickness
Constant Voltage	$\downarrow a$	Constant	$\downarrow a$
Constant Field	$\downarrow a$	$\downarrow a$	$\downarrow a$

**Negative Effects:**

- **Short channel effects:** Threshold voltage roll-off
- **Hot carrier effects:** Device degradation
- **Gate leakage:** Increased tunneling current
- **Process variations:** Manufacturing challenges
- **Power density:** Heat dissipation issues

**Mnemonic:** "SHGPP - Short channel, Hot carrier, Gate leakage, Process, Power"


**Question 2(a) [3 marks]**

Implement  $Y' = (AB' + A'B)$  using CMOS.

**Answer:**

**Logic Analysis:**

$$Y' = (AB' + A'B) = A \oplus B \text{ (XOR function)}$$

 **CMOS Implementation:****Truth Table:**

A	B	AB'	A'B	Y'
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

**Mnemonic:** "XOR needs complementary switching"

## Question 2(b) [4 marks]

Explain enhancement load inverter with its circuit diagrams.

**Answer:**

**Circuit Diagram:**

```

VDD
|
+----o VG2
|
+---+ Enhancement
|ME | Load
+----+
|
+----o Vout
|
+---+
|MD | Driver
+----+
|
GND
|
+----o Vin

```

**Configuration:**

Component	Type	Connection
Load (ME)	Enhancement NMOS	Gate connected to VDD
Driver (MD)	Enhancement NMOS	Gate is input

**Operation:**

- **Load transistor:** Acts as active load resistor
- **High output:** Limited by  $V_T$  of load transistor

- **Low output:** Depends on driver strength
- **Disadvantage:** Poor VOH due to threshold drop

### Transfer Characteristics:

- **VOH:**  $V_{DD} - V_T$  (degraded high level)
- **VOL:** Close to ground potential
- **Noise margin:** Reduced due to threshold loss

**Mnemonic:** "ELI - Enhancement Load Inverter has threshold Issues"

## Question 2(c) [7 marks]


Explain Voltage Transfer Characteristic of inverter.

Answer:

VTC Parameters:

Parameter	Description	Ideal Value
VOH	Output High Voltage	VDD
VOL	Output Low Voltage	0V
VIH	Input High Voltage	VDD/2
VIL	Input Low Voltage	VDD/2
VM	Switching Threshold	VDD/2

VTC Curve:

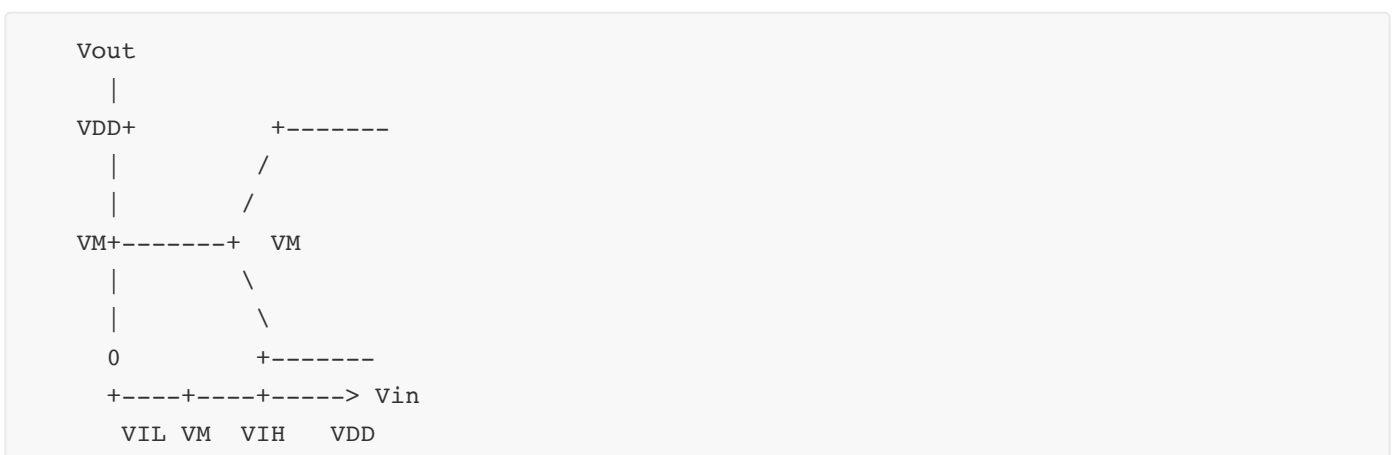

**Noise Margins:**

- **NMH** =  $V_{OH} - V_{IH}$  (High noise margin)
- **NML** =  $V_{IL} - V_{OL}$  (Low noise margin)

**Regions:**

- **Region 1:** Input low, output high
- **Region 2:** Transition region
- **Region 3:** Input high, output low

**Quality Metrics:**

- **Sharp transition:** Better noise immunity
- **Symmetric switching:**  $V_M = V_{DD}/2$
- **Full swing:**  $V_{OH} = V_{DD}$ ,  $V_{OL} = 0$

**Mnemonic:** "VTC shows VOICE -  $V_{OH}$ ,  $V_{OL}$ , Input thresholds, Characteristics, Everything"

## Question 2(a) OR [3 marks]

**Explain NAND2 gate using CMOS.**

**Answer:**

**CMOS NAND2 Circuit:**



**Truth Table:**

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**Operation:**

- **PMOS network:** Parallel connection (pull-up)
- **NMOS network:** Series connection (pull-down)
- **Output low:** Only when both inputs high

**Mnemonic:** "NAND - Not AND, Parallel PMOS, Series NMOS"

## Question 2(b) OR [4 marks]

Explain operating mode and VTC of Resistive load inverter circuit.

**Answer:**

**Circuit Configuration:**

```

VDD
|
R (Load Resistor)
|
+----o Vout
|
+--+--+
|MN | NMOS Driver
+----+
|
GND
|
+----o Vin

```

**Operating Modes:**

Input State	NMOS State	Output
Vin = 0	OFF	VOH = VDD
Vin = VDD	ON	VOL = $R \cdot ID / (R + RDS)$

**VTC Characteristics:**

- **VOH:** Excellent (VDD)



- **VOL:** Depends on R and RDS ratio
- **Power consumption:** Static current when input high
- **Transition:** Gradual due to resistive load

#### Design Trade-offs:

- **Large R:** Better VOL, slower switching
- **Small R:** Faster switching, higher power
- **Area:** Resistor occupies significant space


**Mnemonic:** "RLI - Resistive Load has Inevitable power consumption"

## Question 2(c) OR [7 marks]

Draw CMOS inverter and explain its operation with VTC.

Answer:


CMOS Inverter Circuit:

 

Operation Regions:

Vin Range	PMOS	NMOS	Vout	Region
0 to VTN	ON	OFF	VDD	1
**VTN to VDD-	VTP	**	ON	ON
**VDD-	VTP	to VDD**	OFF	ON

VTC Analysis:

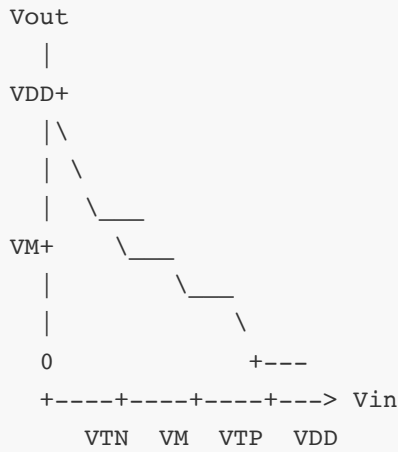

**Key Features:**

- **Zero static power:** No DC current path
- **Full swing:**  $V_{OH} = V_{DD}$ ,  $V_{OL} = 0V$
- **High noise margins:**  $N_{MH} = N_{ML} \approx 0.4V_{DD}$
- **Sharp transition:** High gain in transition region

**Design Considerations:**

- **$\beta$  ratio:**  $\beta_N/\beta_P$  for symmetric switching
- **Threshold matching:**  $V_{TN} \approx |V_{TP}|$  preferred

**Mnemonic:** "CMOS has Zero Static Power with Full Swing"

### Question 3(a) [3 marks]

Realize  $Y = (\bar{A} + \bar{B})\bar{C} + \bar{D} + \bar{E}$  using depletion load.

**Answer:**

**Logic Simplification:**

$$Y = (\bar{A} + \bar{B})\bar{C} + \bar{D} + \bar{E} = \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{D} + \bar{E}$$

**Depletion Load Implementation:**



| | | | |  
GND GND GND GND GND

**Pull-down Network:**

- **Series:**  $\bar{A}\bar{C}$  path and  $\bar{B}\bar{C}$  path
- **Parallel:** All paths connected in parallel
- **Implementation:** Requires proper transistor sizing

**Mnemonic:** "Depletion Load with Parallel pull-down Paths"

**Question 3(b) [4 marks]**

**Write a short note on FPGA.**

**Answer:**

**FPGA Definition:**

**Field Programmable Gate Array** - Reconfigurable integrated circuit.

**Architecture Components:**

Component	Function
CLB	Configurable Logic Block
IOB	Input/Output Block
Interconnect	Routing resources
Switch Matrix	Connection points

**Programming Technologies:**

- **SRAM-based:** Volatile, fast reconfiguration
- **Antifuse:** Non-volatile, one-time programmable
- **Flash-based:** Non-volatile, reprogrammable

**Applications:**

- **Prototyping:** Digital system development
- **DSP:** Signal processing applications
- **Control systems:** Industrial automation
- **Communications:** Protocol implementation

**Advantages vs ASIC:**

- **Flexibility:** Reconfigurable design
- **Time-to-market:** Faster development
- **Cost:** Lower for small volumes

- **Risk:** Reduced design risk


**Mnemonic:** "FPGA - Flexible Programming Gives Advantages"

## Question 3(c) [7 marks]

**Draw and explain Y chart design flow.**

**Answer:**

**Y-Chart Diagram:**

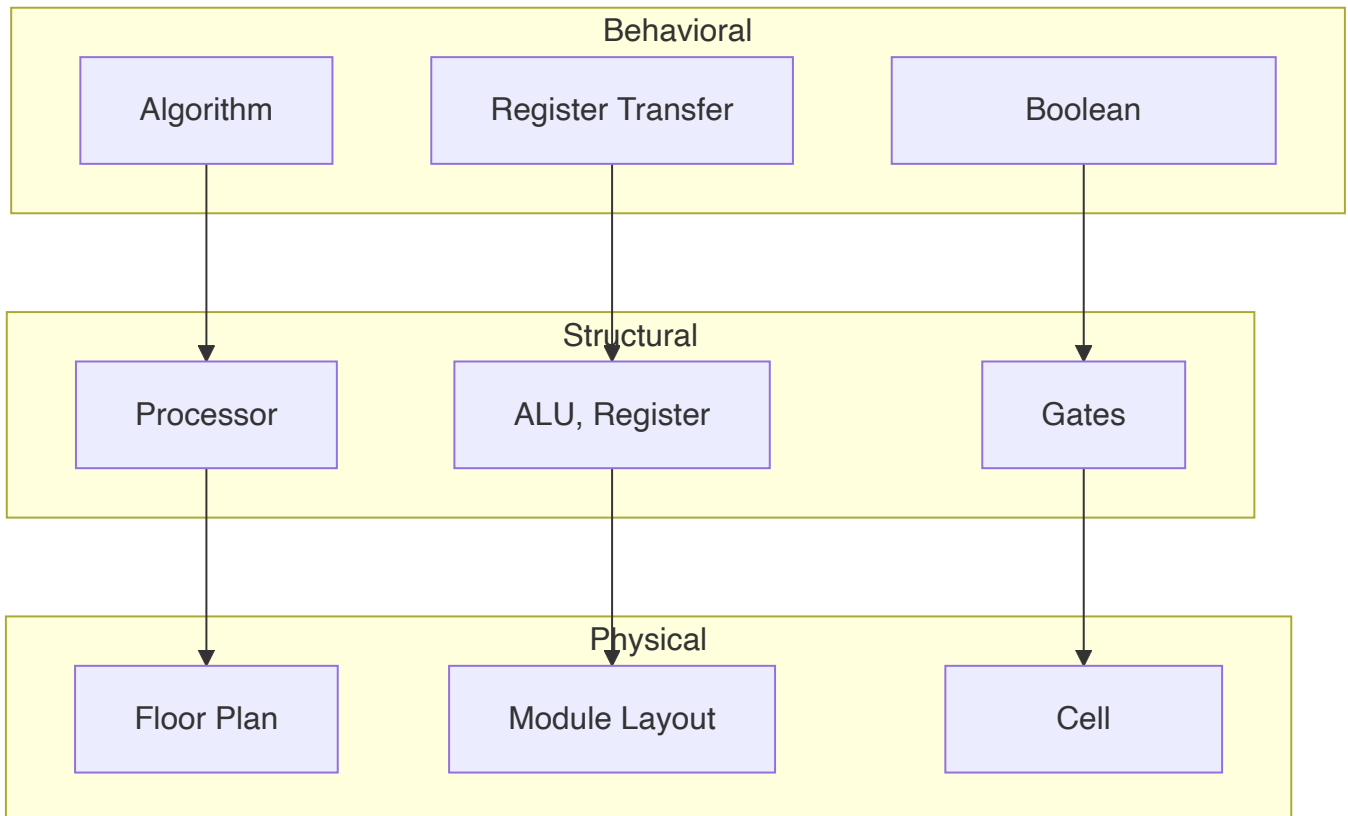

**Design Domains:**

Domain	Levels	Description
<b>Behavioral</b>	Algorithm → RT → Boolean	What the system does
<b>Structural</b>	Processor → ALU → Gates	How system is constructed
<b>Physical</b>	Floor plan → Layout → Cells	Physical implementation

**Design Flow Process:**

- **Top-down:** Start from behavioral, move to physical
- **Bottom-up:** Build from components upward
- **Mixed approach:** Combination of both methods

**Abstraction Levels:**

- **System level:** Highest abstraction
- **RT level:** Register transfer operations
- **Gate level:** Boolean logic implementation
- **Layout level:** Physical geometry

**Design Verification:**

- **Horizontal:** Between domains at same level
- **Vertical:** Between levels in same domain


**Mnemonic:** "Y-Chart: Behavioral, Structural, Physical - BSP domains"

## Question 3(a) OR [3 marks]

Explain NOR2 gate using depletion load.

**Answer:**

**Depletion Load NOR2 Circuit:**

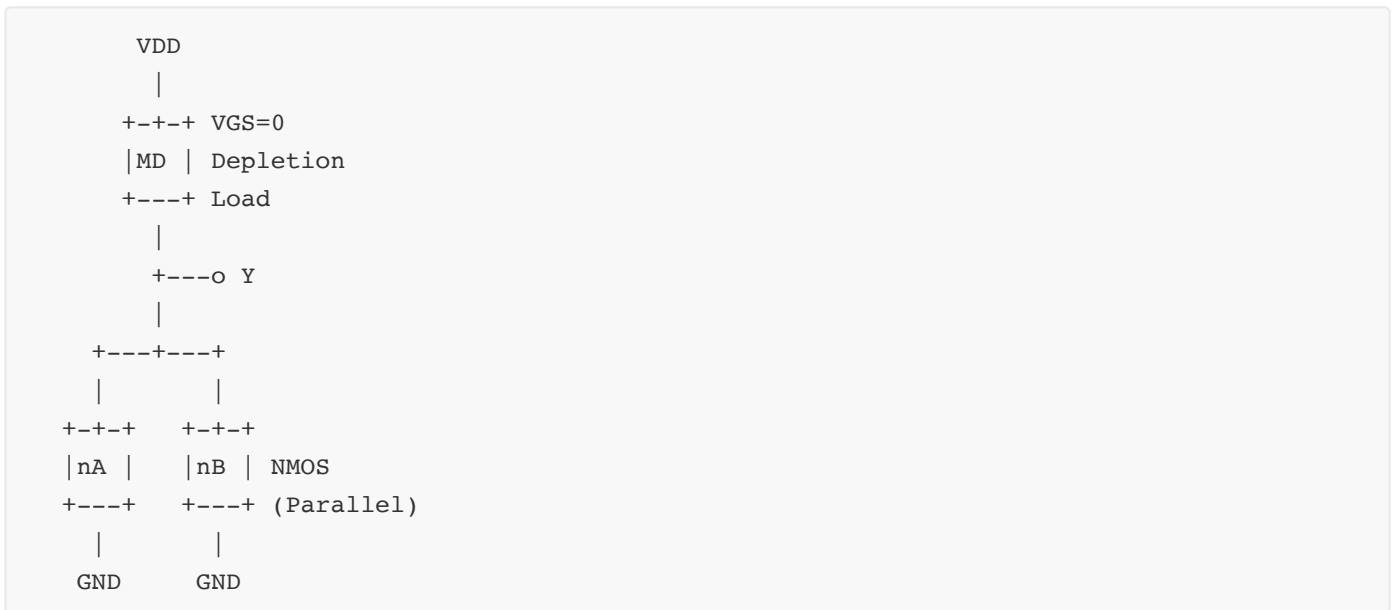

**Truth Table:**

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

**Operation:**

- **Both inputs low:** Both NMOS OFF,  $Y = VDD$
- **Any input high:** Corresponding NMOS ON,  $Y = VOL$
- **Load transistor:** Provides pull-up current

**Mnemonic:** "NOR with Depletion - Parallel NMOS pull-down"

## Question 3(b) OR [4 marks]

Compare full custom and semi-custom design styles.

Answer:

Comparison Table:

Parameter	Full Custom	Semi-Custom
Design Time	Long (6-18 months)	Short (2-6 months)
Performance	Optimal	Good
Area	Minimum	Moderate
Power	Optimized	Acceptable
Cost	High NRE	Lower NRE
Flexibility	Maximum	Limited
Risk	High	Lower

**Full Custom Characteristics:**

- **Every transistor:** Manually designed and placed
- **Layout optimization:** Maximum density achieved
- **Applications:** High-volume, performance-critical

**Semi-Custom Types:**

- **Gate Array:** Pre-defined transistor array
- **Standard Cell:** Library of pre-designed cells
- **FPGA:** Field programmable logic

**Design Flow Comparison:**

- **Full Custom:** Specification → Schematic → Layout → Verification
- **Semi-Custom:** Specification → HDL → Synthesis → Place & Route


**Mnemonic:** "Full Custom - Maximum control, Semi-Custom - Speed compromise"


## Question 3(c) OR [7 marks]

**Draw and explain ASIC design flow in detail.**

**Answer:**

**ASIC Design Flow:**

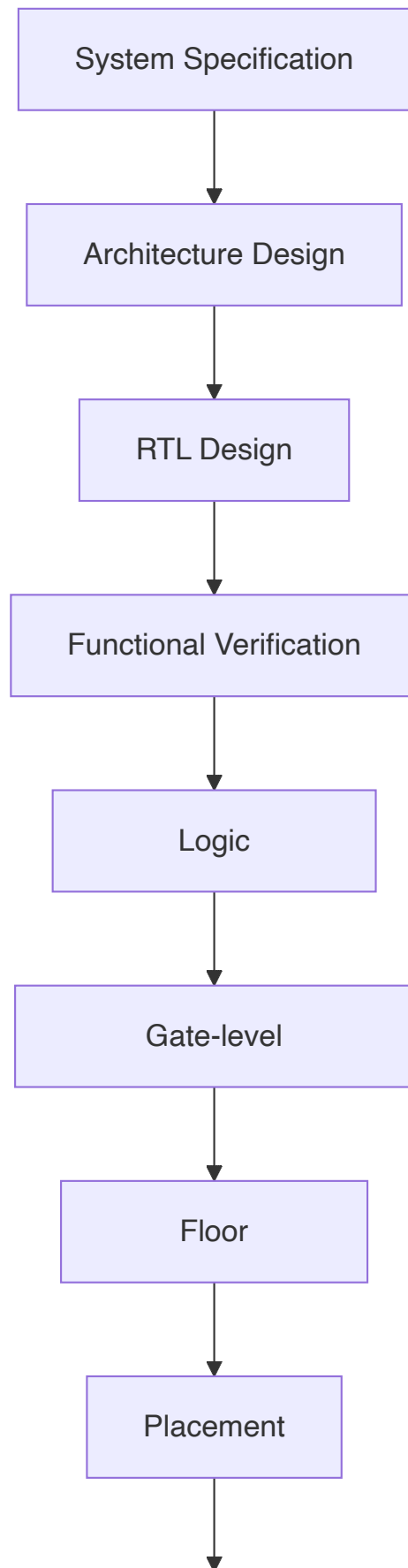

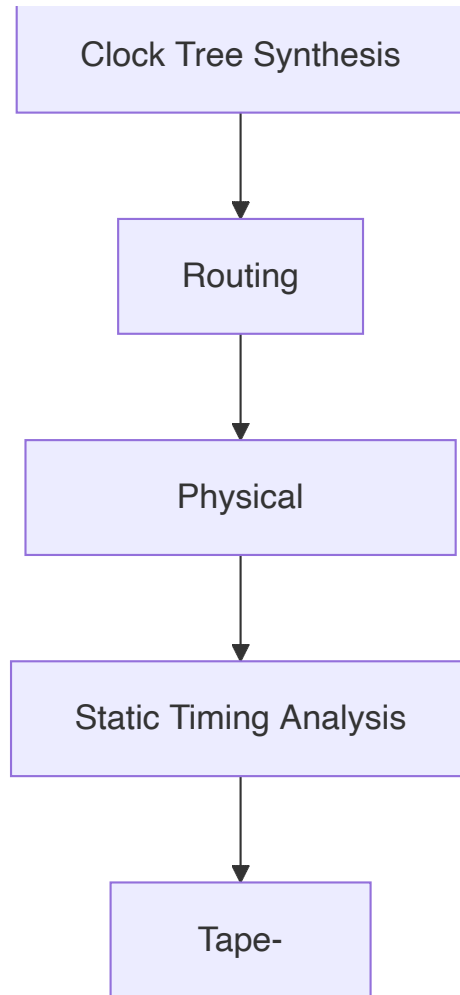

### Design Stages:

Stage	Description	Tools/Methods
<b>RTL Design</b>	Hardware description	Verilog/VHDL
<b>Synthesis</b>	Convert RTL to gates	Logic synthesis tools
<b>Floor Planning</b>	Chip area allocation	Floor planning tools
<b>Placement</b>	Position gates/blocks	Placement algorithms
<b>Routing</b>	Connect placed elements	Routing algorithms

### Verification Steps:

- **Functional:** RTL simulation and verification
- **Gate-level:** Post-synthesis simulation
- **Physical:** DRC, LVS, antenna checks
- **Timing:** STA for setup/hold violations

### Design Constraints:

- **Timing:** Clock frequency requirements



- **Area:** Silicon area limitations
- **Power:** Power consumption targets
- **Test:** Design for testability

**Sign-off Checks:**

- **DRC:** Design Rule Check
- **LVS:** Layout Versus Schematic
- **STA:** Static Timing Analysis
- **Power:** Power integrity analysis

**Mnemonic:** "ASIC flow: RTL → Synthesis → Physical → Verification"

## Question 4(a) [3 marks]


Implement the logic function  $G = (A(D+E)+BC)\bar{}$  using CMOS

**Answer:**

**Logic Analysis:**

$$G = (A(D+E)+BC)\bar{}$$

**CMOS Implementation:**

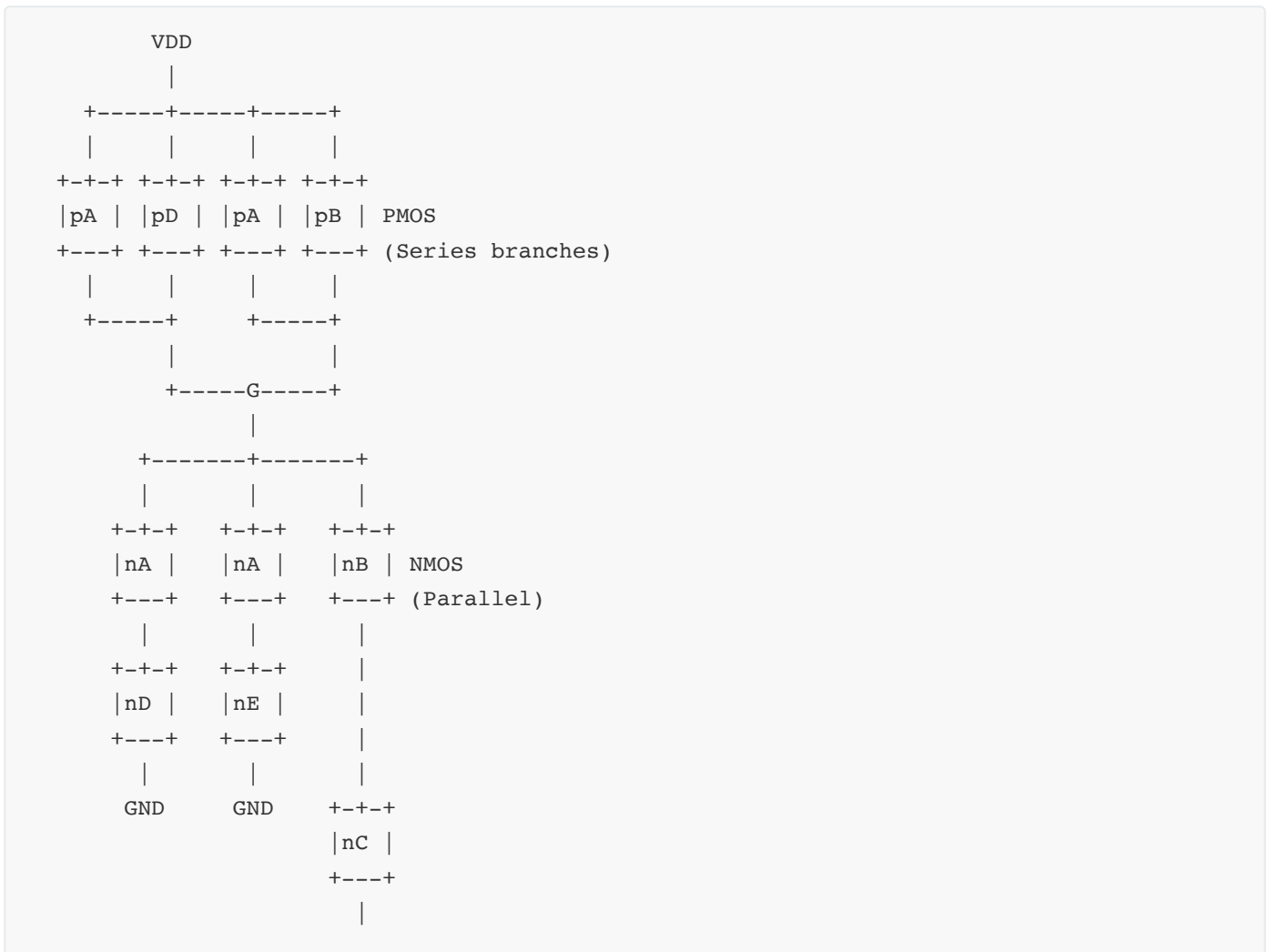

GND

**Network Configuration:**

- **PMOS:** Series implementation of complement
- **NMOS:** Parallel implementation of original function

**Mnemonic:** "Complex CMOS - PMOS series, NMOS parallel"

**Question 4(b) [4 marks]**

Write a Verilog code for 3 bit parity checker.

**Answer:**

**Verilog Code:**

```

module parity_checker_3bit(
    input [2:0] data_in,
    output parity_even,
    output parity_odd
);

// Even parity checker
assign parity_even = ^data_in;

// Odd parity checker
assign parity_odd = ~(^data_in);

// Alternative implementation
/*
assign parity_even = data_in[0] ^ data_in[1] ^ data_in[2];
assign parity_odd = ~(data_in[0] ^ data_in[1] ^ data_in[2]);
*/

endmodule

```

**Truth Table:**

Input [2:0]	Number of 1s	Even Parity	Odd Parity
000	0	0	1
001	1	1	0
010	1	1	0
011	2	0	1
100	1	1	0
101	2	0	1
110	2	0	1
111	3	1	0

**Key Features:**

- **XOR reduction:**  $\text{^data\_in}$  gives even parity
- **Complement:**  $\text{~}(\text{^data\_in})$  gives odd parity

**Mnemonic:** "Parity Check: XOR all bits"

## Question 4(c) [7 marks]

**Implement:**

1)  $G = (AD + BC + EF)$  using CMOS [3 marks]


2)  $Y' = (ABCD + EF(G+H) + J)$  using CMOS [4 marks]

**Answer:**

**Part 1:  $G = (AD + BC + EF)$  [3 marks]**

**CMOS Circuit:**



 

**Part 2:  $Y' = (ABCD + EF(G+H)+ J)$  [4 marks]**

This requires a complex implementation with multiple stages:

**Stage 1:** Implement  $(G+H)$

**Stage 2:** Implement  $EF(G+H)$

**Stage 3:** Combine all terms

**Simplified approach using transmission gates and multiple stages would be more practical for this complex function.**

**Mnemonic:** "Complex functions need staged implementation"

**Question 4(a) OR [3 marks]**

**Explain AOI logic with example.**


**Answer:**


**AOI Definition:**

**AND-OR-Invert** logic implements functions of form:  $Y = (AB + CD + \dots)$

**Example:**  $Y = (AB + CD)$

**AOI Implementation:**

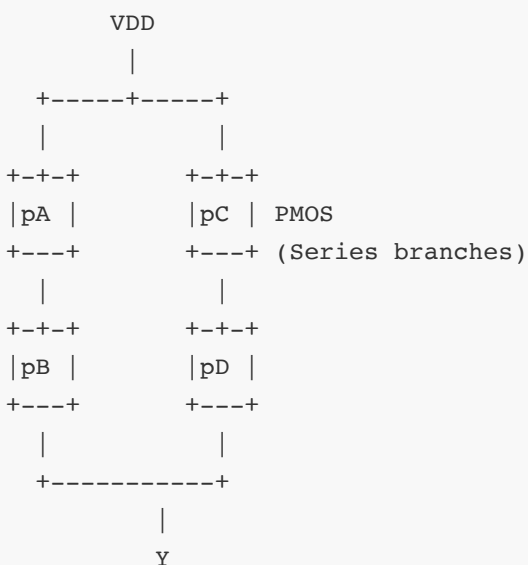

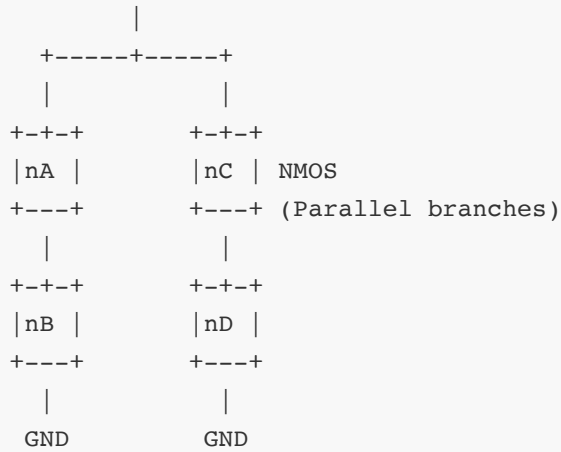**Advantages:**

- **Single stage:** Direct implementation
- **Fast:** No propagation through multiple levels
- **Area efficient:** Fewer transistors than separate gates

**Applications:**

- **Complex gates:** Multi-input functions
- **Speed-critical paths:** Reduced delay

**Mnemonic:** "AOI - AND-OR-Invert in one stage"

## Question 4(b) OR [4 marks]

Write Verilog Code for 4-bit Serial IN Parallel out shift register.

**Answer:**

**Verilog Code:**

```
module sipo_4bit(
    input clk,
    input reset,
    input serial_in,
    output reg [3:0] parallel_out
);

always @(posedge clk or posedge reset) begin
    if (reset) begin
        parallel_out <= 4'b0000;
    end else begin
        // Shift left and insert new bit at LSB
        parallel_out <= {parallel_out[2:0], serial_in};
    end
end

endmodule
```

**Testbench Example:**

```

module tb_sipo_4bit;
    reg clk, reset, serial_in;
    wire [3:0] parallel_out;

    sipo_4bit dut(.clk(clk), .reset(reset),
                .serial_in(serial_in),
                .parallel_out(parallel_out));

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        reset = 1; serial_in = 0;
        #10 reset = 0;
        #10 serial_in = 1; // LSB first
        #10 serial_in = 0;
        #10 serial_in = 1;
        #10 serial_in = 1; // MSB
        #20 $finish;
    end
endmodule

```

**Operation Timeline:**

Clock	Serial_in	Parallel_out
1	1	0001
2	0	0010
3	1	0101
4	1	1011


**Mnemonic:** "SIPO - Serial In, Parallel Out with shift left"

**Question 4(c) OR [7 marks]**


Implement clocked NOR2 SR latch and D-latch using CMOS.

Answer:


Clocked NOR2 SR Latch:

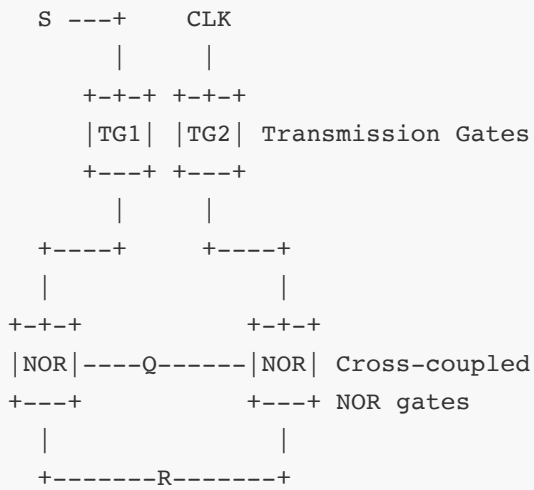

**D-Latch Implementation:**

 

**CMOS D-Latch Circuit:**

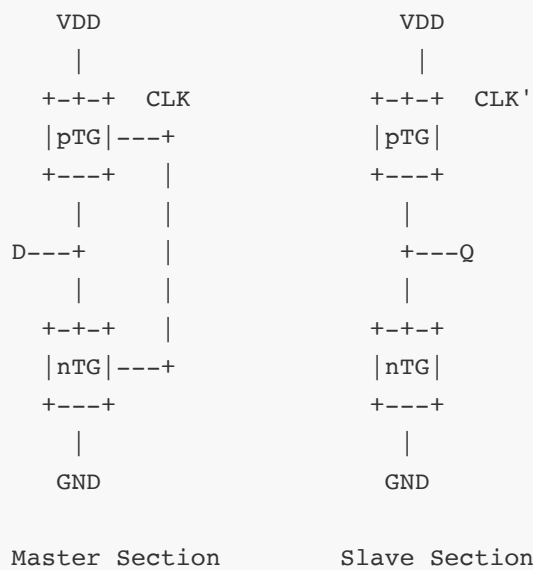

**Operation:**

- **CLK = 1:** Master transparent, slave holds
- **CLK = 0:** Master holds, slave transparent
- **Data transfer:** On clock edge

**Truth Table for SR Latch:**

S	R	CLK	Q	Q'
0	0	1	Hold	Hold
0	1	1	0	1
1	0	1	1	0
1	1	1	Invalid	Invalid

**Mnemonic:** "Clocked latches use transmission gates for timing control"

### Question 5(a) [3 marks]

**Draw the stick diagram for  $Y = (PQ + U)'$  using CMOS considering Euler path approach.**


**Answer:**

**Logic Analysis:**

$Y = (PQ + U)'$  requires PMOS:  $(PQ)' \cdot U' = (P' + Q') \cdot U'$

NMOS:  $PQ + U$

**Stick Diagram:**

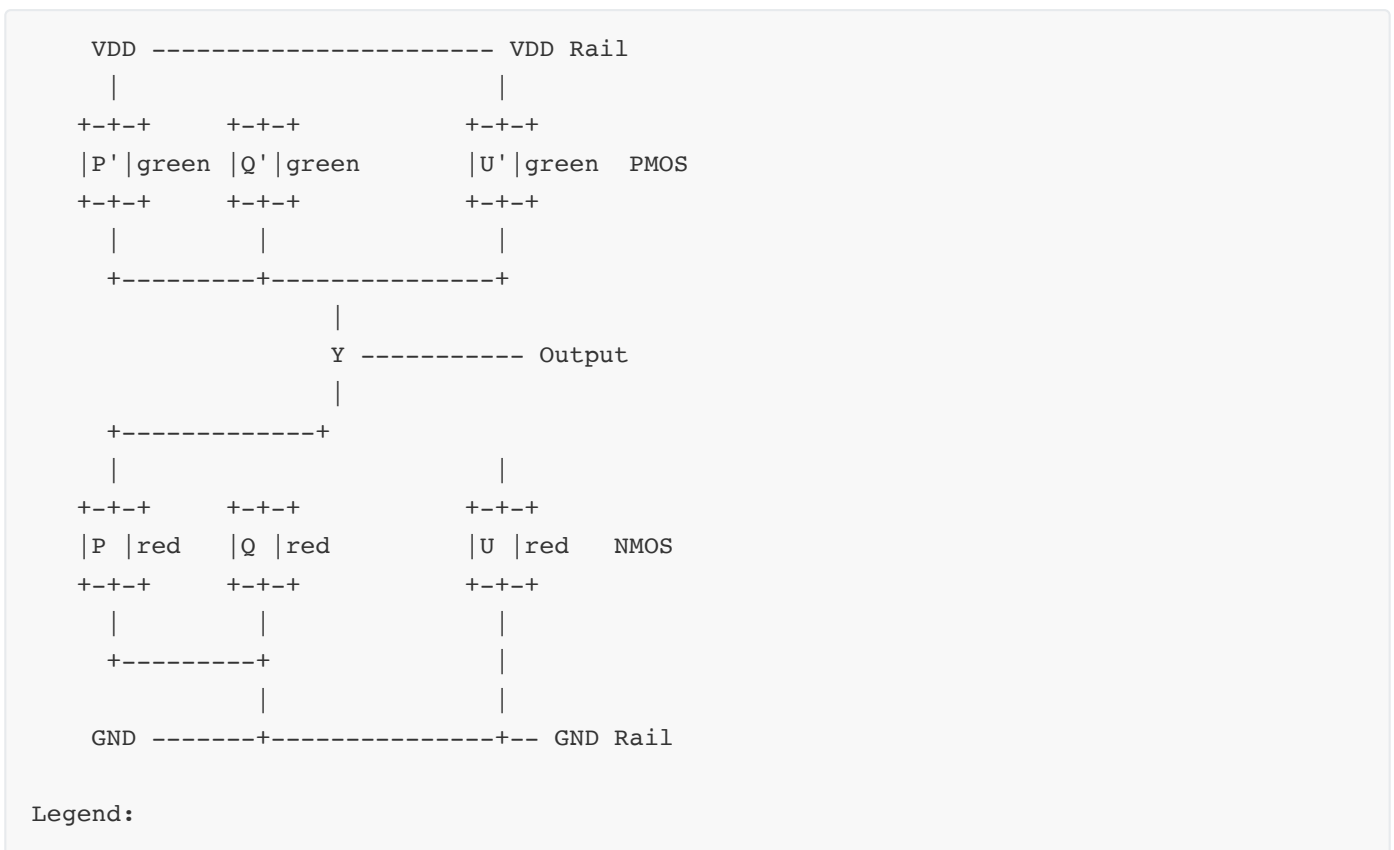



- Green: P-diffusion (PMOS)
- Red: N-diffusion (NMOS)
- Blue: Polysilicon (Gates)
- Metal: Interconnections

**Euler Path:**

1. **PMOS:** P' → Q' (series), then parallel to U'
2. **NMOS:** P → Q (series), then parallel to U
3. **Optimal routing:** Minimizes crossovers

**Layout Considerations:**

- **Diffusion breaks:** Minimize for better performance
- **Contact placement:** Proper VDD/GND connections
- **Metal routing:** Avoid DRC violations

**Mnemonic:** "Stick diagram shows physical layout with Euler path optimization"

## Question 5(b) [4 marks]

**Implement 8×1 multiplexer using Verilog**

**Answer:**

**Verilog Code:**

```

module mux_8x1(
    input [7:0] data_in,    // 8 data inputs
    input [2:0] select,    // 3-bit select signal
    output reg data_out    // Output
);

always @(*) begin
    case (select)
        3'b000: data_out = data_in[0];
        3'b001: data_out = data_in[1];
        3'b010: data_out = data_in[2];
        3'b011: data_out = data_in[3];
        3'b100: data_out = data_in[4];
        3'b101: data_out = data_in[5];
        3'b110: data_out = data_in[6];
        3'b111: data_out = data_in[7];
        default: data_out = 1'b0;
    endcase
end

endmodule

```

**Alternative Implementation:**

```

module mux_8x1_dataflow(
    input [7:0] data_in,
    input [2:0] select,
    output data_out
);

assign data_out = data_in[select];

endmodule

```

**Truth Table:**

Select[2:0]	Output
000	data_in[0]
001	data_in[1]
010	data_in[2]
011	data_in[3]
100	data_in[4]
101	data_in[5]
110	data_in[6]
111	data_in[7]

**Testbench:**

```

module tb_mux_8x1;
    reg [7:0] data_in;
    reg [2:0] select;
    wire data_out;

    mux_8x1 dut(.data_in(data_in), .select(select), .data_out(data_out));

    initial begin
        data_in = 8'b10110100;
        for (int i = 0; i < 8; i++) begin
            select = i;
            #10;
            $display("Select=%d, Output=%b", select, data_out);
        end
    end
endmodule

```

**Mnemonic:** "MUX selects one of many inputs based on select lines"

## Question 5(c) [7 marks]

Implement full adder using behavioral modeling style in Verilog.

Answer:

Verilog Code:

```

module full_adder_behavioral(
    input A,
    input B,
    input Cin,
    output reg Sum,
    output reg Cout
);

// Behavioral modeling using always block
always @(*) begin
    case ({A, B, Cin})
        3'b000: begin Sum = 1'b0; Cout = 1'b0; end
        3'b001: begin Sum = 1'b1; Cout = 1'b0; end
        3'b010: begin Sum = 1'b1; Cout = 1'b0; end
        3'b011: begin Sum = 1'b0; Cout = 1'b1; end
        3'b100: begin Sum = 1'b1; Cout = 1'b0; end
        3'b101: begin Sum = 1'b0; Cout = 1'b1; end
        3'b110: begin Sum = 1'b0; Cout = 1'b1; end
        3'b111: begin Sum = 1'b1; Cout = 1'b1; end
        default: begin Sum = 1'b0; Cout = 1'b0; end
    endcase
end

endmodule

```

Alternative Behavioral Style:

```

module full_adder_behavioral_alt(
    input A, B, Cin,
    output reg Sum, Cout
);

always @(*) begin
    {Cout, Sum} = A + B + Cin;
end

endmodule

```

Truth Table:

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Testbench:**

```

module tb_full_adder;
    reg A, B, Cin;
    wire Sum, Cout;

    full_adder_behavioral dut(.A(A), .B(B), .Cin(Cin),
        .Sum(Sum), .Cout(Cout));

    initial begin
        $monitor("A=%b B=%b Cin=%b | Sum=%b Cout=%b",
            A, B, Cin, Sum, Cout);

        {A, B, Cin} = 3'b000; #10;
        {A, B, Cin} = 3'b001; #10;
        {A, B, Cin} = 3'b010; #10;
        {A, B, Cin} = 3'b011; #10;
        {A, B, Cin} = 3'b100; #10;
        {A, B, Cin} = 3'b101; #10;
        {A, B, Cin} = 3'b110; #10;
        {A, B, Cin} = 3'b111; #10;

        $finish;
    end
endmodule

```

**Behavioral Features:**

- **Always block:** Describes behavior, not structure
- **Case statement:** Truth table implementation
- **Automatic synthesis:** Tools generate optimized circuit

**Mnemonic:** "Behavioral modeling describes what circuit does, not how"

## Question 5(a) OR [3 marks]


Implement NOR2 gate CMOS circuit with its stick diagram.

Answer:

CMOS NOR2 Circuit:



Stick Diagram:

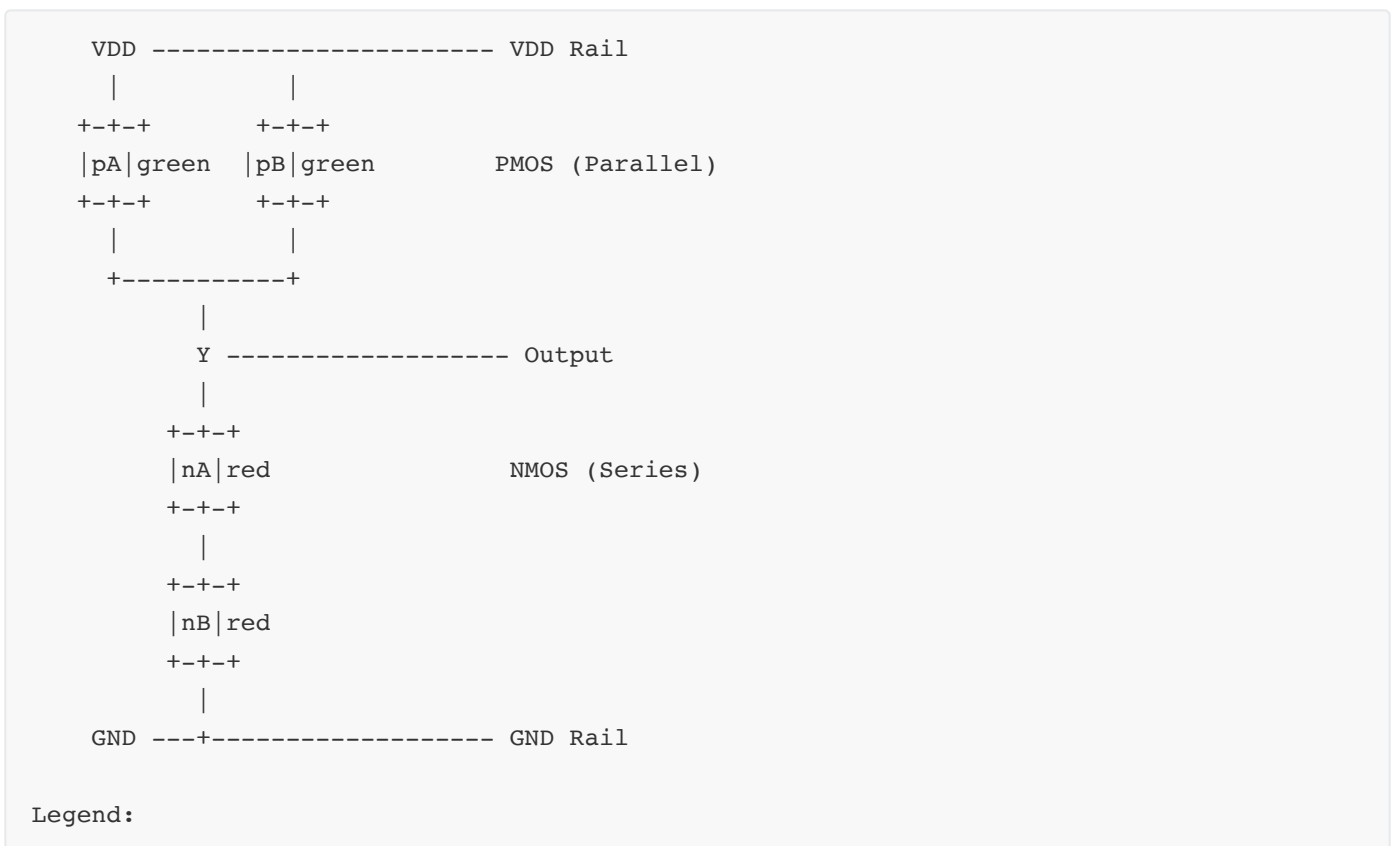

- Green: P-diffusion
- Red: N-diffusion
- Blue: Polysilicon gates
- Metal: Connections

**Layout Rules:**

- **PMOS:** Parallel connection for pull-up
- **NMOS:** Series connection for pull-down
- **Contacts:** Proper VDD/GND connections
- **Spacing:** Meet minimum design rules

**Mnemonic:** "NOR gate: Parallel PMOS, Series NMOS"

## Question 5(b) OR [4 marks]

---

**Implement 4 bit up counter using Verilog**

**Answer:**

**Verilog Code:**

```

module counter_4bit_up(
    input clk,
    input reset,
    input enable,
    output reg [3:0] count
);

always @(posedge clk or posedge reset) begin
    if (reset) begin
        count <= 4'b0000;
    end else if (enable) begin
        if (count == 4'b1111) begin
            count <= 4'b0000; // Rollover
        end else begin
            count <= count + 1;
        end
    end
    // If enable is low, hold current value
end

endmodule

```

**Enhanced Version with Overflow:**

```

module counter_4bit_enhanced(
    input clk,
    input reset,
    input enable,

```

```

output reg [3:0] count,
output overflow
);

always @(posedge clk or posedge reset) begin
    if (reset) begin
        count <= 4'b0000;
    end else if (enable) begin
        count <= count + 1; // Natural rollover
    end
end

assign overflow = (count == 4'b1111) & enable;

endmodule

```

### Count Sequence:

Clock	Count[3:0]	Decimal
1	0000	0
2	0001	1
3	0010	2
...	...	...
15	1110	14
16	1111	15
17	0000	0 (rollover)

### Testbench:

```

module tb_counter_4bit;
    reg clk, reset, enable;
    wire [3:0] count;

    counter_4bit_up dut(.clk(clk), .reset(reset),
                       .enable(enable), .count(count));

    // Clock generation
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    // Test sequence
    initial begin
        reset = 1; enable = 0;
    end
endmodule

```

```

    #10 reset = 0; enable = 1;
    #200 enable = 0; // Stop counting
    #20 enable = 1; // Resume
    #100 $finish;
end

// Monitor
always @(posedge clk) begin
    $display("Time=%t Count=%d", $time, count);
end
endmodule

```

**Mnemonic:** "Up counter: increment on each clock when enabled"

## Question 5(c) OR [7 marks]

**Implement 3:8 decoder using behavioral modeling style in Verilog.**

**Answer:**

**Verilog Code:**

```

module decoder_3x8_behavioral(
    input [2:0] address, // 3-bit address input
    input enable, // Enable signal
    output reg [7:0] decode_out // 8-bit decoded output
);

always @(*) begin
    if (enable) begin
        case (address)
            3'b000: decode_out = 8'b00000001; // Y0
            3'b001: decode_out = 8'b00000010; // Y1
            3'b010: decode_out = 8'b00000100; // Y2
            3'b011: decode_out = 8'b00001000; // Y3
            3'b100: decode_out = 8'b00010000; // Y4
            3'b101: decode_out = 8'b00100000; // Y5
            3'b110: decode_out = 8'b01000000; // Y6
            3'b111: decode_out = 8'b10000000; // Y7
            default: decode_out = 8'b00000000;
        endcase
    end else begin
        decode_out = 8'b00000000; // All outputs low when disabled
    end
end

endmodule

```

**Alternative Implementation:**



```

module decoder_3x8_shift(
    input [2:0] address,
    input enable,
    output [7:0] decode_out
);

assign decode_out = enable ? (8'b00000001 << address) : 8'b00000000;

endmodule

```

**Truth Table:**

Enable	Address[2:0]	decode_out[7:0]
0	XXX	00000000
1	000	00000001
1	001	00000010
1	010	00000100
1	011	00001000
1	100	00010000
1	101	00100000
1	110	01000000
1	111	10000000

**Testbench:**

```

module tb_decoder_3x8;
    reg [2:0] address;
    reg enable;
    wire [7:0] decode_out;

    decoder_3x8_behavioral dut(.address(address), .enable(enable),
        .decode_out(decode_out));

    initial begin
        $monitor("Enable=%b Address=%b | Output=%b",
            enable, address, decode_out);

        // Test with enable = 0
        enable = 0;
        for (int i = 0; i < 8; i++) begin
            address = i;
            #10;
        end
    end
endmodule

```

```
end

// Test with enable = 1
enable = 1;
for (int i = 0; i < 8; i++) begin
    address = i;
    #10;
end

$finish;
end
endmodule
```

### Applications:

- **Memory addressing:** Select one of 8 memory locations
- **Device selection:** Enable one of 8 peripheral devices
- **Demultiplexing:** Route single input to selected output

### Design Features:

- **One-hot encoding:** Only one output high at a time
- **Enable control:** Global enable/disable functionality
- **Full decoding:** All possible input combinations handled

**Mnemonic:** "3:8 Decoder - 3 inputs select 1 of 8 outputs"